

# Experiment 1

## Introduction to Semiconductors

### *Diode Characteristics*

#### **INTRODUCTION:**

Semiconductors are the cornerstone of modern electronic devices, with diodes playing a critical role by allowing current to flow in one direction. This experiment investigates the voltage-current (V-I) characteristics of a silicon junction diode to understand its behavior under different biasing conditions. Utilizing Multisim software for circuit simulation and a bench setup for empirical measurement, the experiment aims to compare the forward bias region's theoretical expectations, where the diode conducts electricity after surpassing the silicon diode's characteristic turn-on voltage, with practical observations. This comparison is expected to demonstrate the practical application of semiconductor theory, as detailed in section 2-2 of the course textbook, and offer insight into the nuances of diode functionality through graphical analysis of the V-I relationship.

#### **BENCH PARTS AND EQUIPMENT LIST:**

##### **1. Diodes:**

- Silicon Diode (1N4001)

##### **2. Resistors:**

- 1 k $\Omega$  resistor

#### **Bench Equipment:**

##### **1. Power Supply:**

- DC Voltage Source capable of supplying a variable voltage from 1V to 15V.

##### **2. Measurement Instruments:**

- Multimeter (for measuring voltage across and current through the diode).
- Oscilloscope (to observe and analyze the V-I characteristics of the diode under AC conditions).

##### **3. Signal Generators:**


- Function Generator (capable of producing a sine wave signal, with an amplitude of 10 Vpp at a frequency of 1 kHz for AC analysis).

#### 4. Prototyping and Interconnect:


- Breadboard or other prototyping board (for assembling the circuit).
- Connecting wires and/or jumper wires (for making electrical connections between components on the breadboard).

### DISCUSSION:

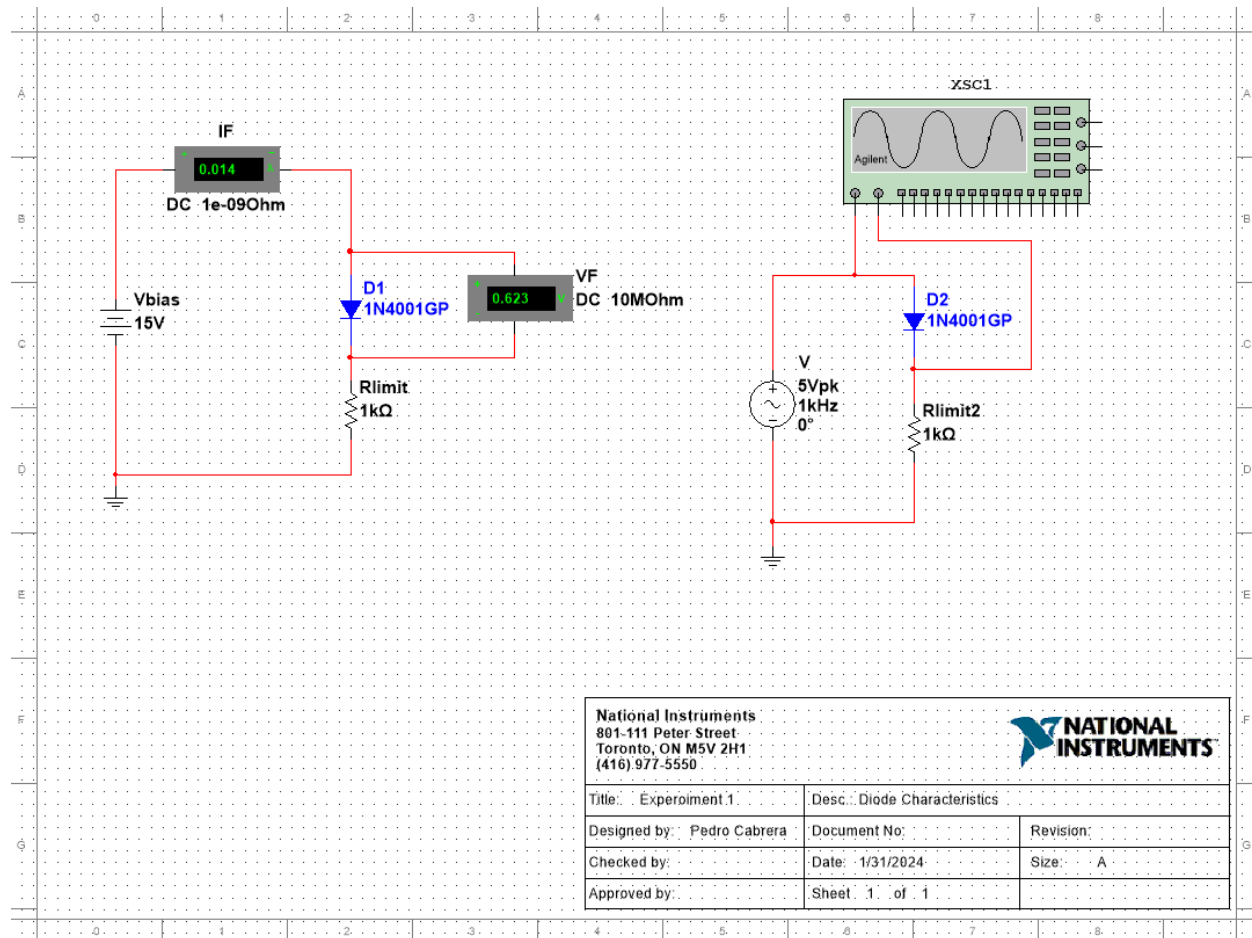
#### Part 1: Multisim DC Circuit Analysis



In the first part of the experiment, we built a DC circuit in Multisim to observe the V-I characteristics of a silicon diode. The bias voltage ( $V_{bias}$ ) was varied in 1V increments from 1V to 15V, and the corresponding forward current ( $I_F$ ) was measured. The diode's behavior agreed with semiconductor theory, exhibiting a threshold voltage near 0.7V, beyond which the current increased significantly, indicating the diode had entered its conducting state. Notably, the simulation allowed for an ideal environment where temperature and manufacturing variances were absent, thus presenting a more idealized diode characteristic curve compared to what one might expect in a physical setup.


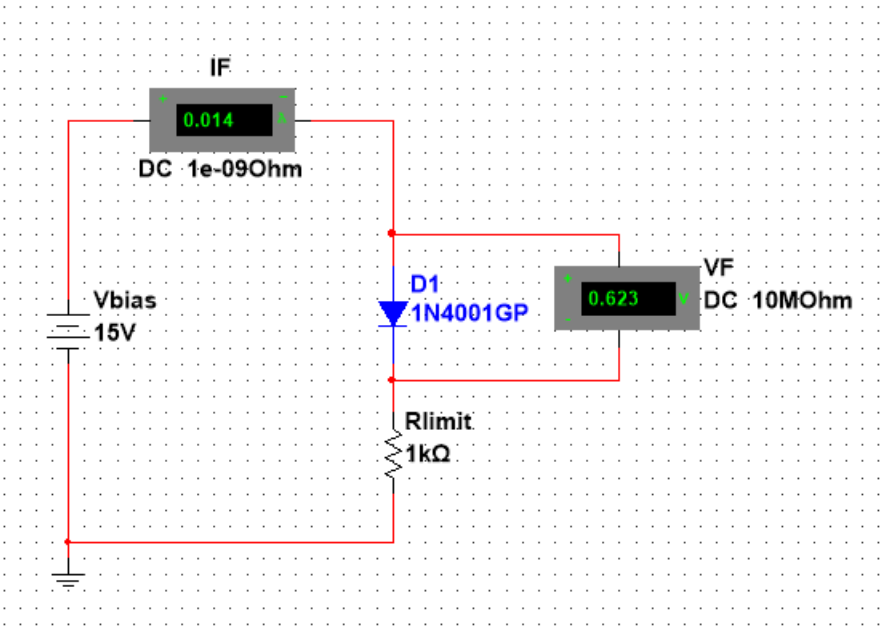


$V_{bias} (V)$	Simulated		Measured		Variance	
	$V_F$	$i_F$	$V_F$	$i_F$	$V_F$	$i_F$
1	422.0E-3	578.0E-6	5.57E-01	5.10E-04	24%	-13%
2	482.0E-3	1.518E-3	6.05E-01	1.45E-03	20%	-5%
3	513.0E-3	2.487E-3	6.28E-01	2.44E-03	18%	-2%
4	534.0E-3	3.467E-3	6.43E-01	3.40E-03	17%	-2%
5	549.0E-3	4.450E-3	6.55E-01	4.37E-03	16%	-2%
6	562.0E-3	5.438E-3	6.63E-01	5.38E-03	15%	-1%
7	572.0E-3	6.429E-3	6.70E-01	6.41E-03	15%	0%
8	581.0E-3	7.419E-3	6.76E-01	7.35E-03	14%	-1%
9	589.0E-3	8.409E-3	6.81E-01	8.42E-03	14%	0%
10	596.0E-3	9.404E-3	6.85E-01	9.43E-03	13%	0%
11	602.0E-3	10.0E-3	6.89E-01	1.04E-02	13%	4%
12	608.0E-3	11.0E-3	6.93E-01	1.14E-02	12%	4%
13	613.0E-3	12.0E-3	6.97E-01	1.24E-02	12%	3%
14	618.0E-3	13.0E-3	7.00E-01	1.34E-02	12%	3%
15	623.0E-3	14.0E-3	7.02E-01	1.44E-02	11%	3%

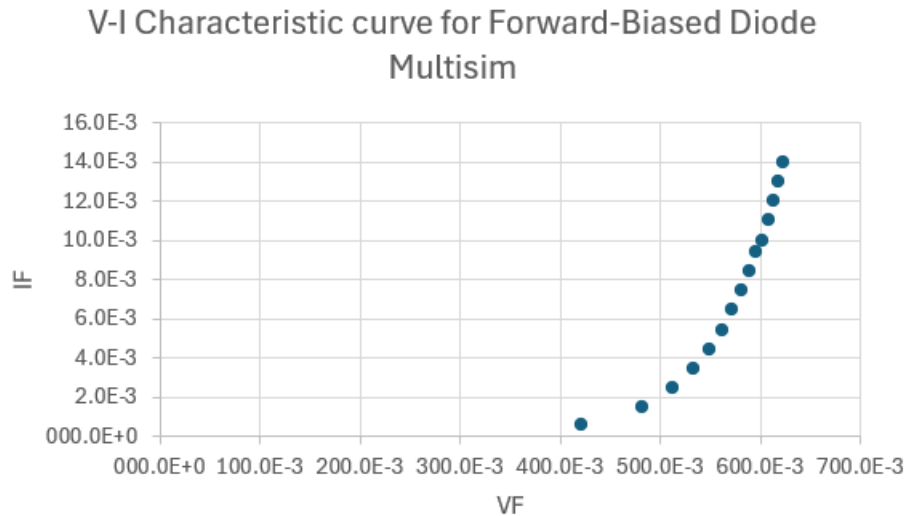
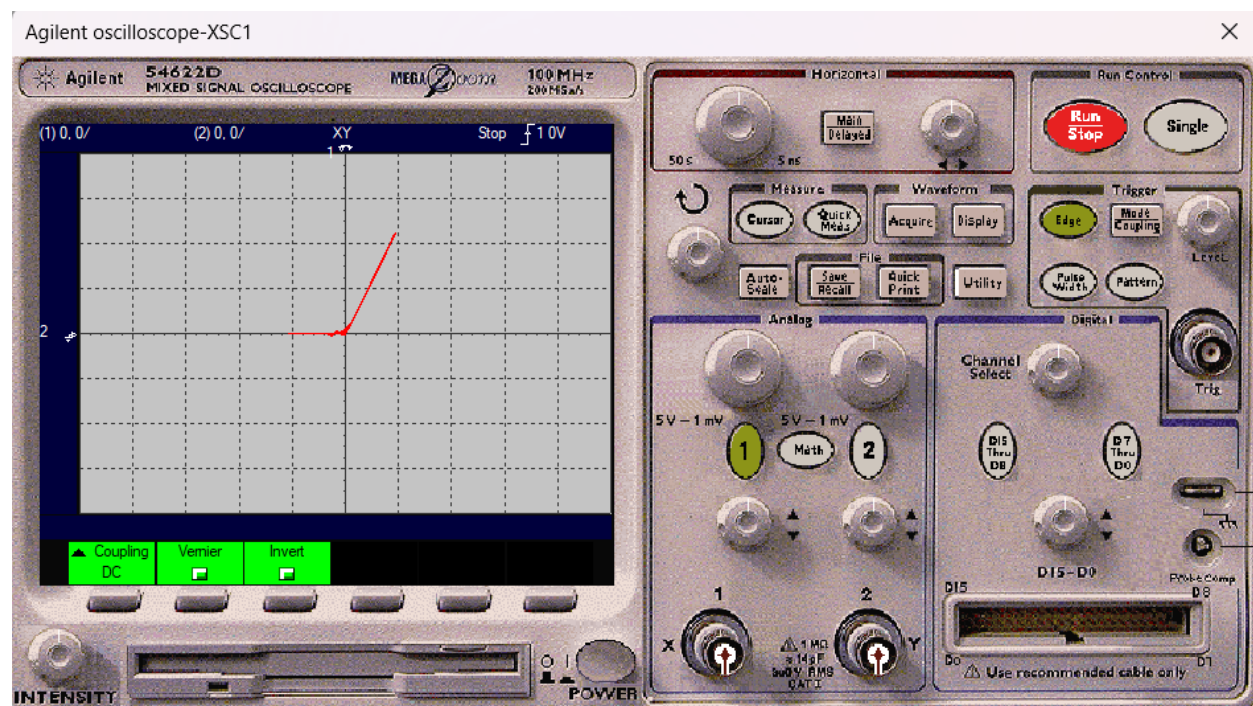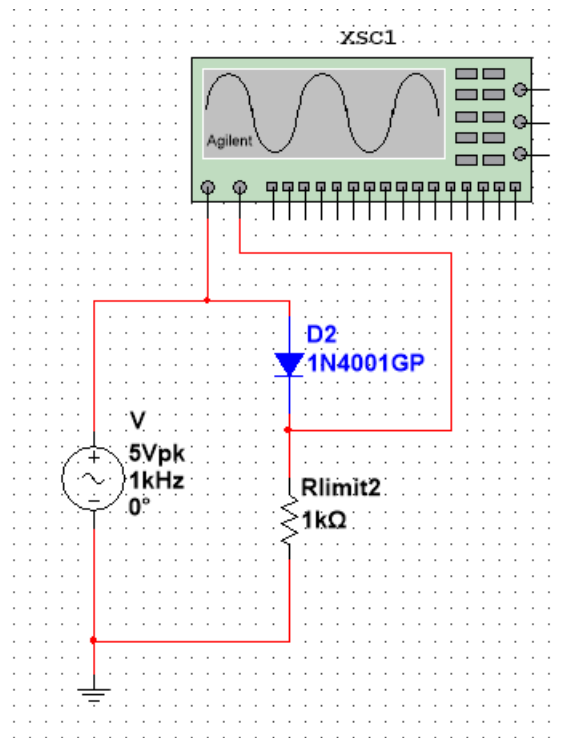
## Part 2: Multisim AC Circuit Analysis


For the AC analysis in Multisim, the circuit used a sine wave from a function generator with a peak voltage of 10V at 1kHz. The oscilloscope displayed distinct half-wave rectification, as only the positive half of the sine wave was allowed to pass, a characteristic inherent to diodes. It was particularly interesting to observe the effect of the diode on the sine wave, confirming its rectifying nature in real-time. The virtual oscilloscope's clean signal display highlighted the advantage of simulation in analyzing ideal circuit behaviors without real-world interference.


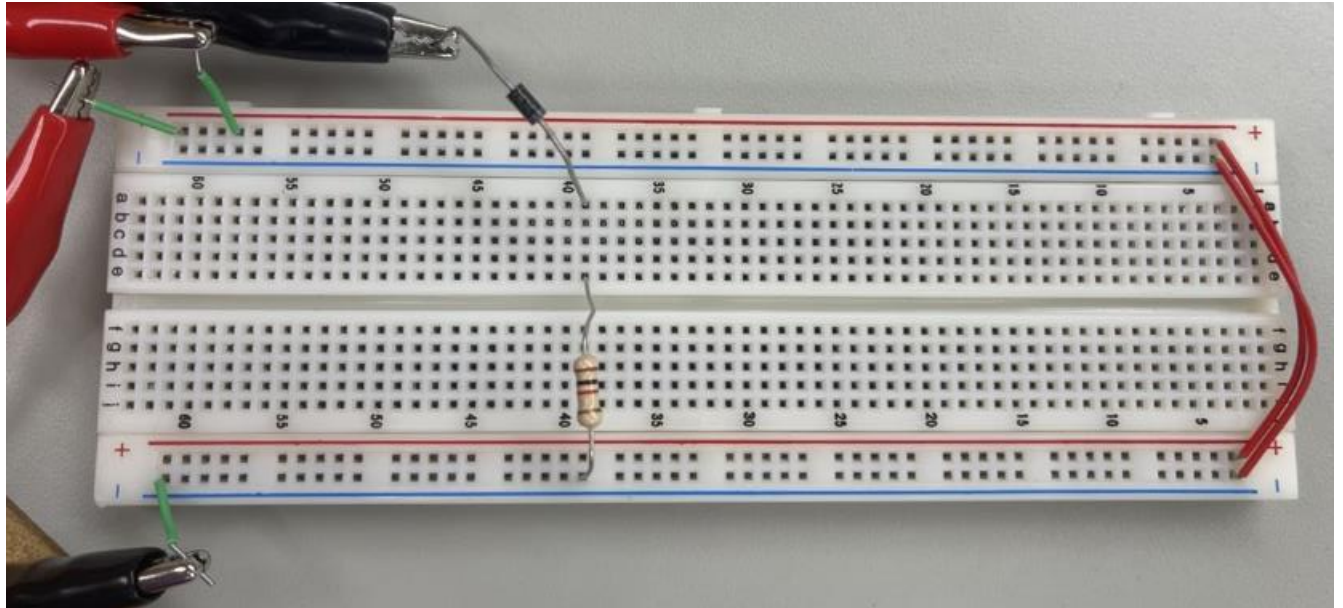
### Part 3: Bench DC Circuit and Excel Graphing Analysis

The bench DC circuit replicated the Multisim setup, using a physical diode and resistor. By varying  $V_{bias}$  manually and measuring the  $V_F$  (forward-bias voltage) and  $I_F$  with a

multimeter, we plotted the V-I curve in Excel. The results showed a steeper curve after the threshold voltage, characteristic of real diodes. This activity underscored the influence of physical factors, such as the diode's temperature sensitivity and manufacturing imperfections, on its operational characteristics, which were not as apparent in the simulation.









\*\* Using DMM to measure  $I_F$  @ 1V



\*\*  $I_F$  @ 7V

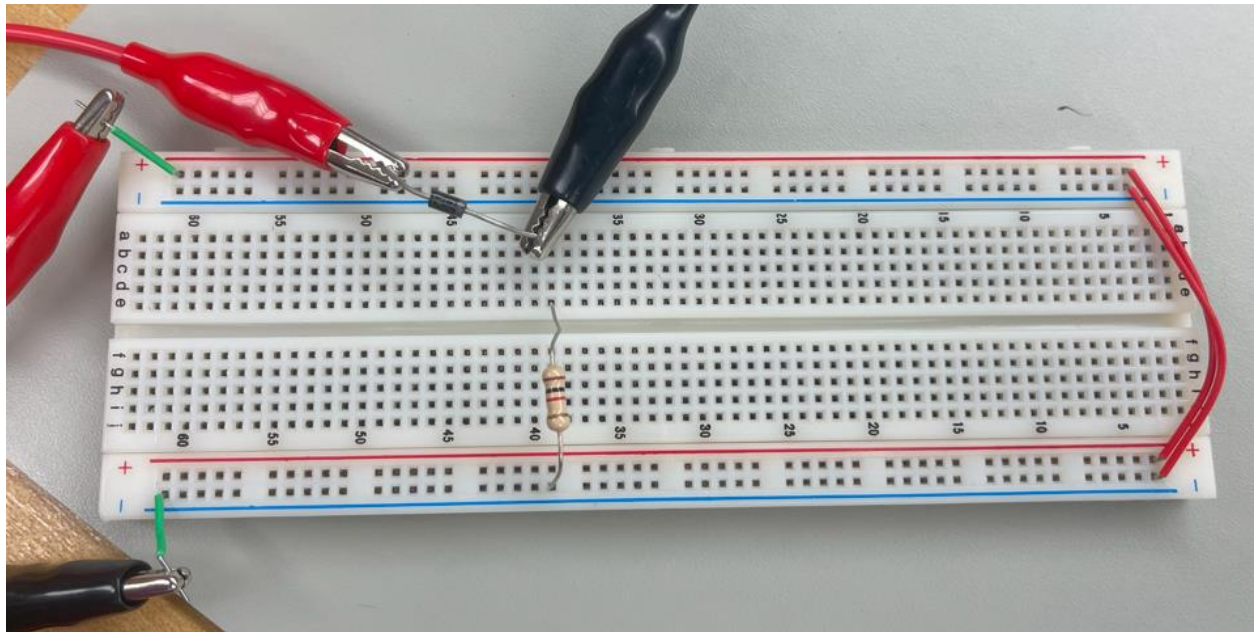

\*\* Getting ready to measure  $V_F$

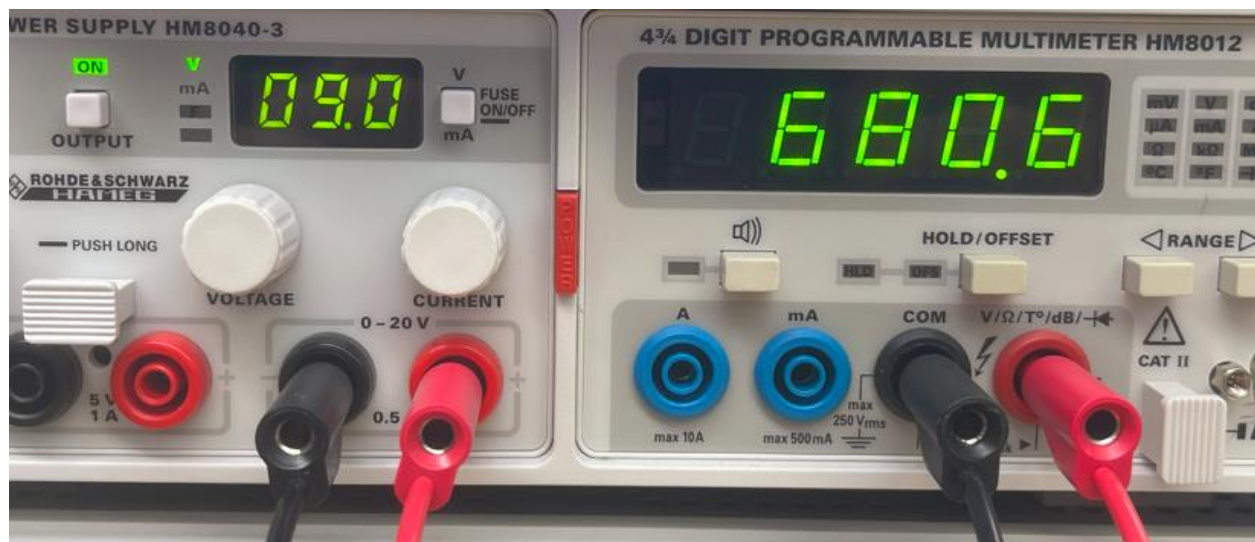


\*\*  $V_F$  @ 9V measuring 680.6 mV



Part 3: Bench DC Circuit and Excel Graphing Analysis  
**Materials:**

- Resistor (1 k $\Omega$ )
- Diode (1N4001)
- DC Voltage Source
- Multimeter

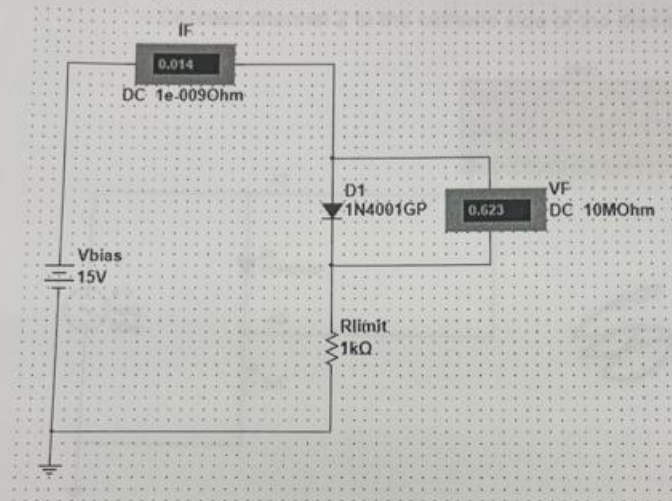
1. Build the following DC circuit on the bench:



2. Vary  $V_{bias}$  from 1 V to 15 V in increments of 1 V
3. Create three columns in Excel:  $V_{bias}$ ,  $V_F$ ,  $I_F$
4. Record  $V_{bias}$ ,  $V_F$ , and  $I_F$  in Excel
5. Graph  $V_F$  on x-axis and  $I_F$  on y-axis in Excel by selecting the  $V_F$  and  $I_F$  data cells and then clicking on "Insert"/"Recommended Charts"/"Scatter" to obtain your "V-I Characteristics Curve for a Forward-Biased Diode"
6. Compare this curve to your Multisim DC Circuit analysis results in Part 1


$V_{\text{bias}} \text{ (V)}$	Simulated		Measured		Variance	
	$V_F$	$i_F$	$V_F$	$i_F$	$V_F$	$i_F$
1	422.0E-3	578.0E-6	5.57E-01	5.10E-04	24%	-13%
2	482.0E-3	1.518E-3	6.05E-01	1.45E-03	20%	-5%
3	513.0E-3	2.487E-3	6.28E-01	2.44E-03	18%	-2%
4	534.0E-3	3.467E-3	6.43E-01	3.40E-03	17%	-2%
5	549.0E-3	4.450E-3	6.55E-01	4.37E-03	16%	-2%
6	562.0E-3	5.438E-3	6.63E-01	5.38E-03	15%	-1%
7	572.0E-3	6.429E-3	6.70E-01	6.41E-03	15%	0%
8	581.0E-3	7.419E-3	6.76E-01	7.35E-03	14%	-1%
9	589.0E-3	8.409E-3	6.81E-01	8.42E-03	14%	0%
10	596.0E-3	9.404E-3	6.85E-01	9.43E-03	13%	0%
11	602.0E-3	10.0E-3	6.89E-01	1.04E-02	13%	4%
12	608.0E-3	11.0E-3	6.93E-01	1.14E-02	12%	4%
13	613.0E-3	12.0E-3	6.97E-01	1.24E-02	12%	3%
14	618.0E-3	13.0E-3	7.00E-01	1.34E-02	12%	3%
15	623.0E-3	14.0E-3	7.02E-01	1.44E-02	11%	3%

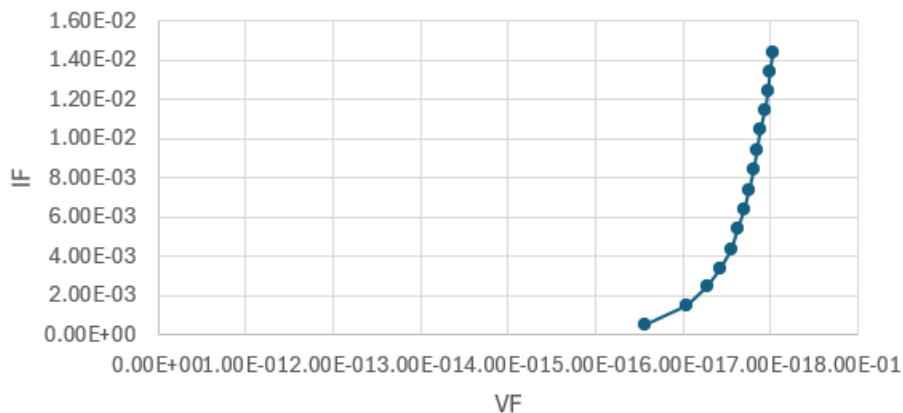V-I Characteristic curve for Forward-Biased Diode  
Bench



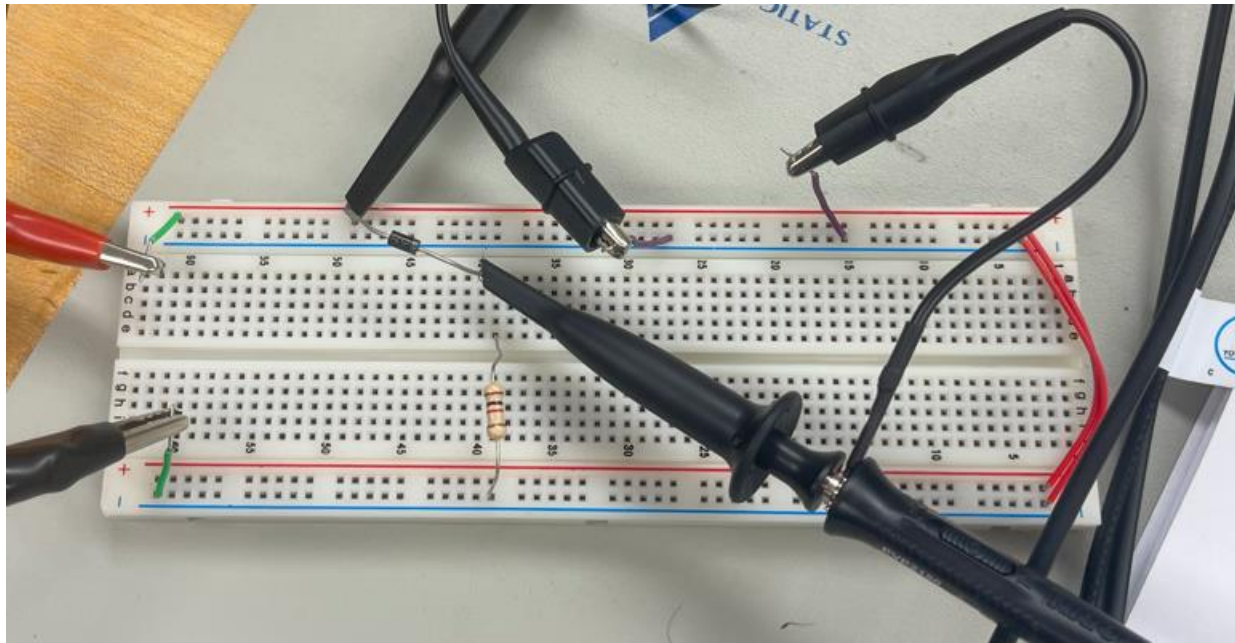
#### Part 4: Bench AC Circuit Analysis


On the bench, the AC circuit used a function generator and an oscilloscope, similar to the simulation, but the real-world implementation provided insights into practical challenges, such as noise and signal integrity. The oscilloscope revealed a V-I characteristic curve with noticeable irregularities compared to the ideal curve seen in Multisim. This part of the experiment was crucial in illustrating the impact of real-world conditions on the diode's performance, offering a tangible contrast to the simulated environment.



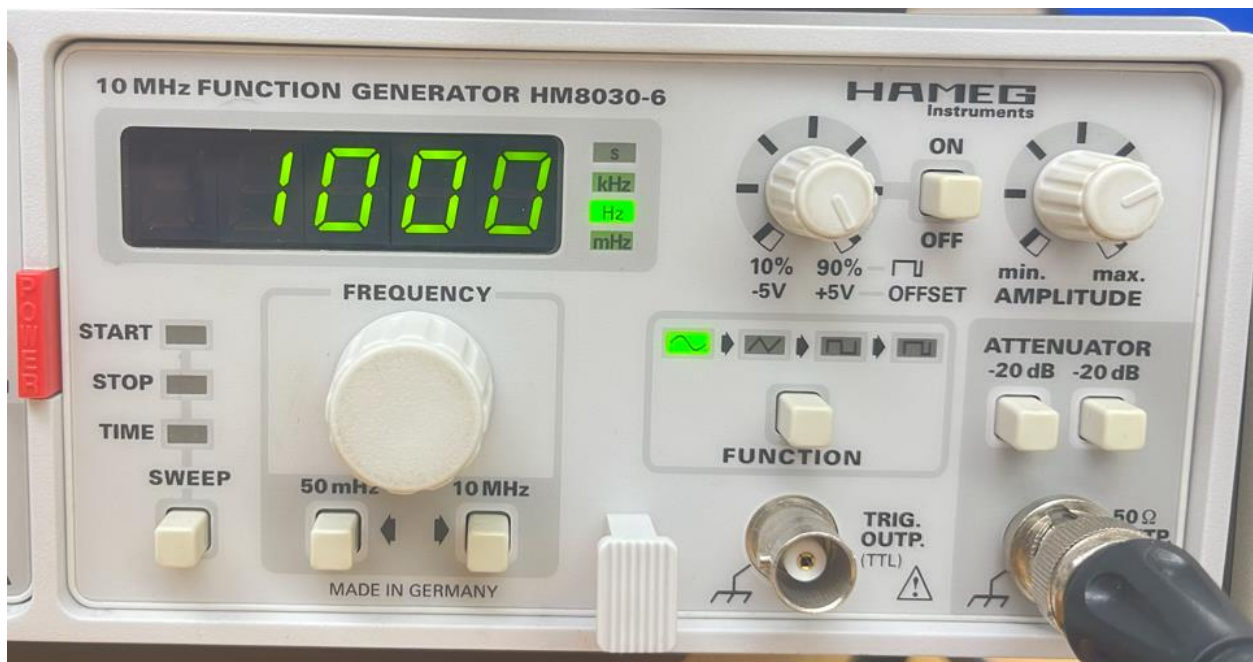\*\* Setting up the circuit with the Signal Generator wires and Oscilloscope probes.



\*\* Verification of the Frequency

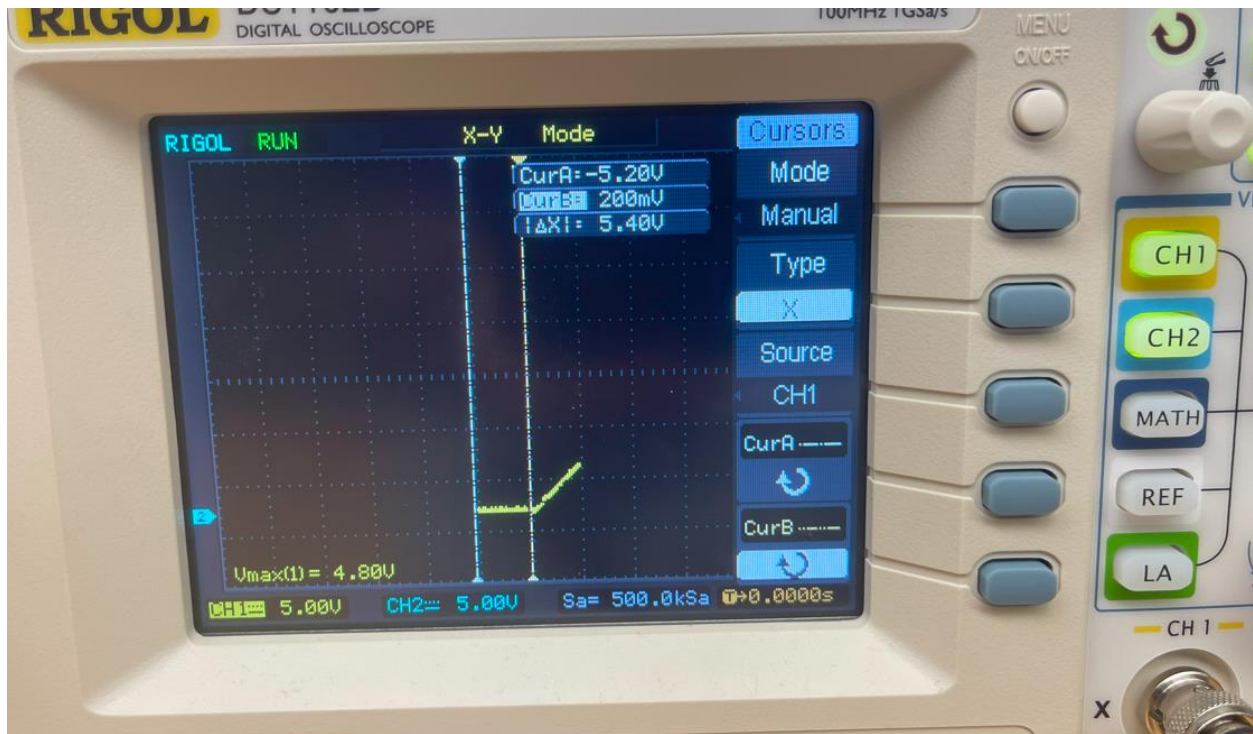

\*\* Bench V-I



☐ Function Generator  
☐ Oscilloscope  
☐ Resistor (1 k $\Omega$ )  
☐ Diode (1N4001)

1. Build the following AC circuit:

Input: Function Generator - Sine Wave, 10 V<sub>pp</sub>, 1 kHz

Output: Oscilloscope – Connect channel 1 to the Anode side of the diode  
 – Connect channel 2 to the cathode side of the diode

To make sure that both oscilloscope probes are set on "1x" and on "DC" coupling, on the Rigol Oscilloscope:

1. Press "CH1"
2. Press top blue button
3. Dial in "DC"
4. Press "CH2"
5. Press top blue button
6. Dial in "DC"

To view the V-I characteristic of the diode curve on the Rigol Oscilloscope:

1. Look under Horizontal section and press "Menu"
2. Select Time Base
3. Use knob to turn to X-Y
4. Press in knob to make selection permanent

## CONCLUSION:

This laboratory experiment provided a comprehensive examination of the voltage-current characteristics of a silicon diode, both through simulation and practical bench work. The exercise reinforced the theoretical principles of diode operation, with Multisim simulations offering an idealized view that closely matched textbook expectations, specifically demonstrating the diode's rectifying nature and its forward bias behavior. Bench experiments further solidified our understanding by introducing the complexities of real-world applications,



such as the effects of temperature and component imperfections, which slightly altered the diode's V-I characteristics. The discrepancies observed between the simulated and actual results emphasize the necessity of hands-on experience in engineering education, as it highlights the nuances that can only be appreciated through physical experimentation. Overall, the experiment successfully bridged the gap between theoretical semiconductor diode behavior and its practical implementation, thereby enhancing our grasp of the fundamental electronic principles critical for the design and analysis of electronic circuits.