

# Experiment 7

## Bipolar Junction Transistor

### ***Voltage Divider Biasing***

#### **Introduction:**

The primary objective of this laboratory exercise is to explore and understand the principles of voltage divider biasing in bipolar junction transistors (BJTs). Voltage divider biasing is a crucial concept in electronic circuits, as it sets the DC operating point which is vital for the linear operation of amplifiers. Through this lab, we aim to establish a stable base voltage for a BJT amplifier circuit, which will allow for consistent performance despite variations in temperature or transistor beta ( $\beta$ ) value. We intend to construct a voltage divider biased circuit and calculate various parameters such as base voltage ( $V_B$ ), collector-emitter voltage ( $V_{CE}$ ), and collector current ( $I_C$ ). By comparing the theoretical computations with the measured results, we will assess the impact of emitter resistance on the operation of the transistor. This hands-on experiment will enhance our comprehension of electronic circuit design and the dynamic behavior of transistors, which is foundational knowledge for more advanced studies in electronics and electrical engineering.

#### **Bench Parts and Equipment List:**

##### 1. Components:

- BJT Transistor (2N3904)
- Resistors:
  - $R_1$ : 10 k $\Omega$
  - $R_2$ : 2.2 k $\Omega$
  - $R_C$ : 3.6 k $\Omega$
  - $R_E$ : 1 k $\Omega$  & 2k $\Omega$

##### 2. Equipment:

- Power Supply
- Multimeter
- Breadboard

**Discussion:**

In analyzing the data collected from both the Multisim simulations and the physical benchwork in the lab, a notable trend emerged regarding the influence of the emitter resistance ( $R_E$ ) on the stability of the transistor's operating point. As  $R_E$  was varied, its impact on the base voltage ( $V_B$ ), collector-emitter voltage ( $V_{CE}$ ), and collector current ( $I_C$ ) was evident. With a  $1\text{k}\Omega R_E$ , the circuit tended to have lower  $V_{CE}$  and  $I_C$  values compared to those with a  $2\text{k}\Omega R_E$ . This aligns with the theoretical expectations, as increasing the emitter resistance should result in a higher  $V_E$  (emitter voltage), thereby reducing  $V_{CE}$  for a given supply voltage ( $V_{CC}$ ). Additionally, the observed increase in  $I_C$  with a larger  $R_E$  suggests a shift in the operating point toward saturation, which is consistent with the common-emitter configuration behavior.

It is also important to consider the practical aspects of component tolerances as observed from the measured resistor values. The discrepancies between nominal and measured resistor values underscore the necessity of accounting for real-world variances in circuit design. These variances could be the reason behind any deviations from the expected theoretical outcomes.

**Table 1**

<b>Resistor</b>	<b>Nominal</b>	<b>Measured</b>
$R_1$	$10\text{k}\Omega$	$9.896\text{k}\Omega$
$R_2$	$2.2\text{k}\Omega$	$2.172\text{k}\Omega$
$R_C$	$3.6\text{k}\Omega$	$3.569\text{k}\Omega$
$R_E$	$1\text{k}\Omega \& 2\text{k}\Omega$	$981.5\text{k}\Omega \& 1.998\text{k}\Omega$



Figure 1

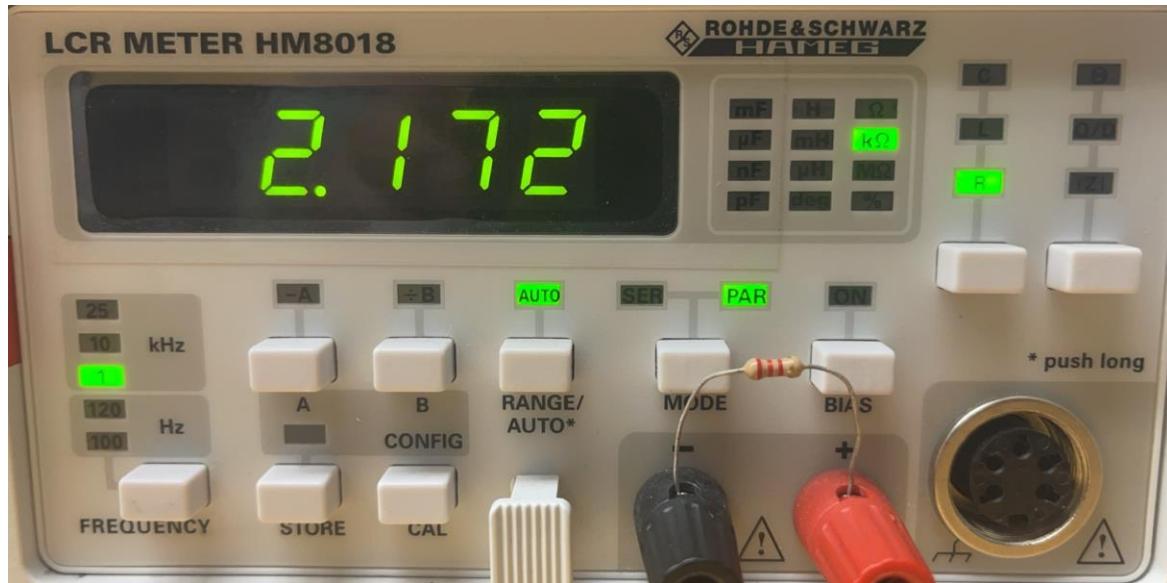


Figure 2



Figure 3



Figure 4

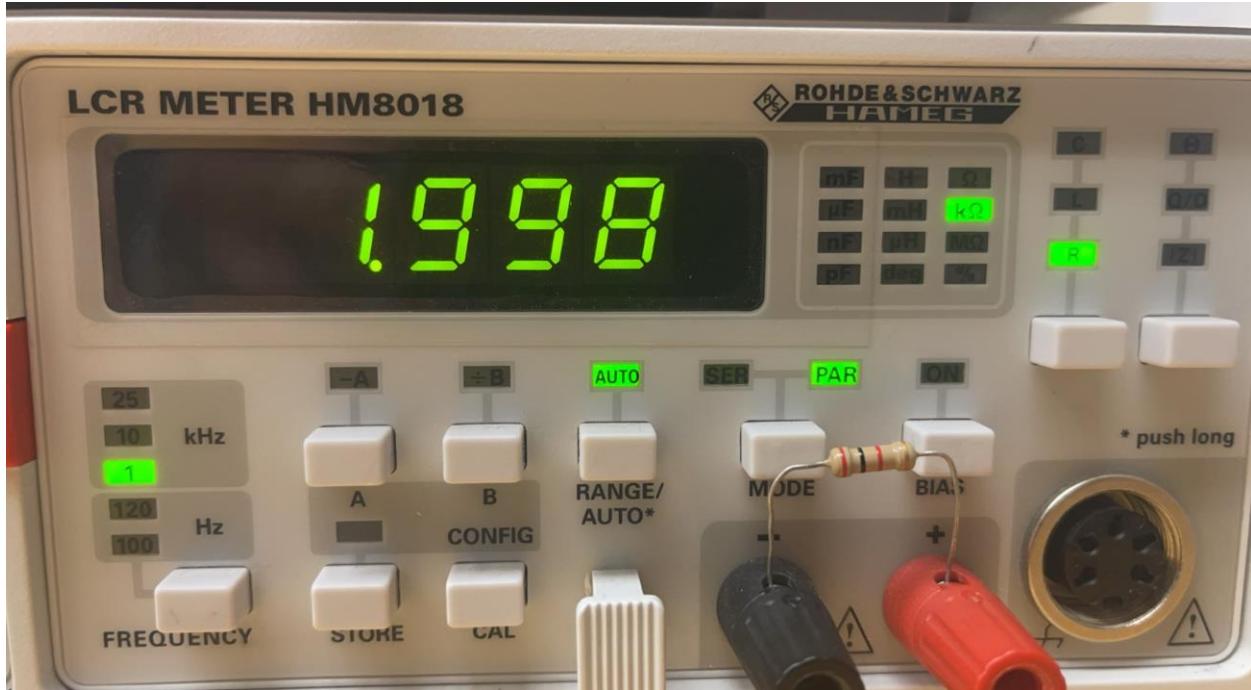


Figure 5

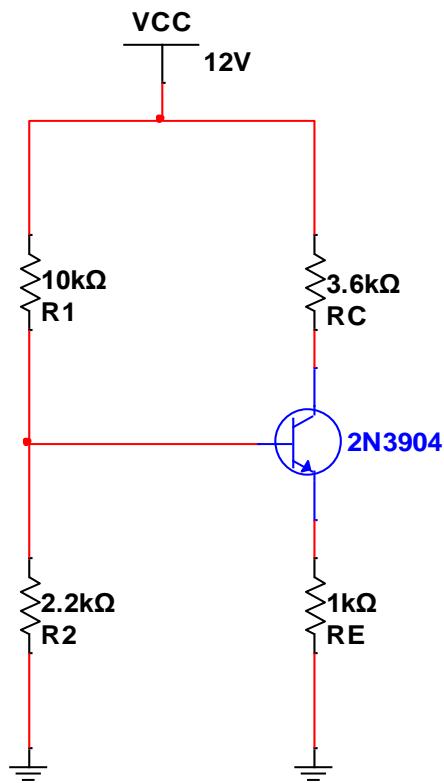


Figure 6



Figure 7

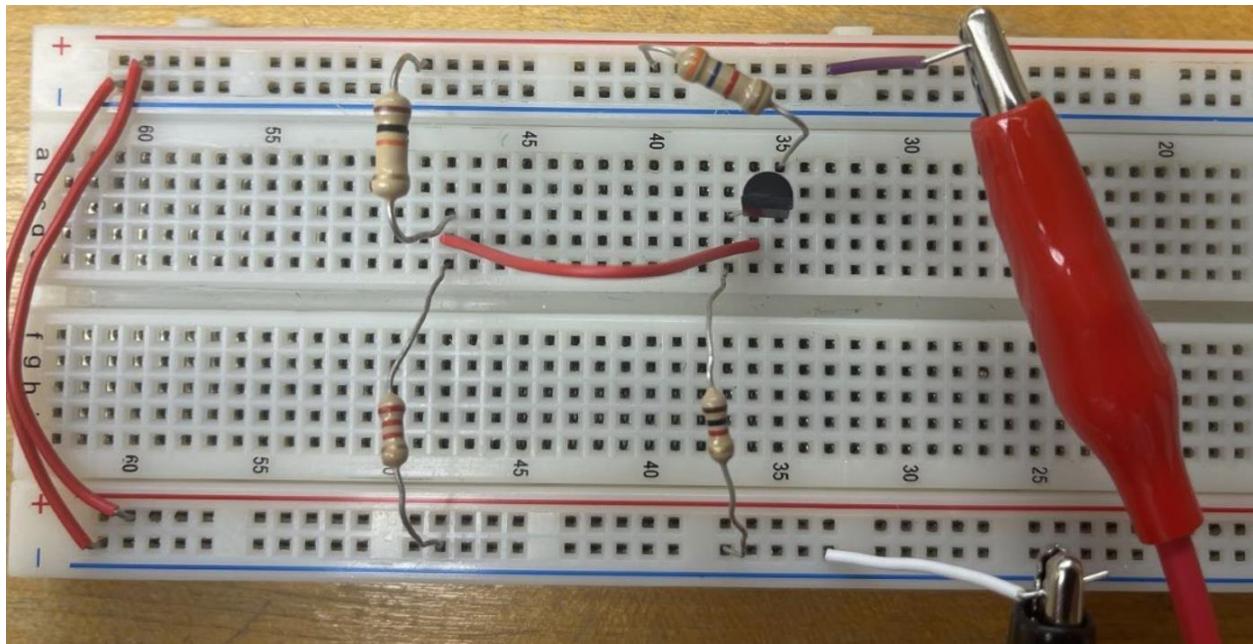


Figure 8

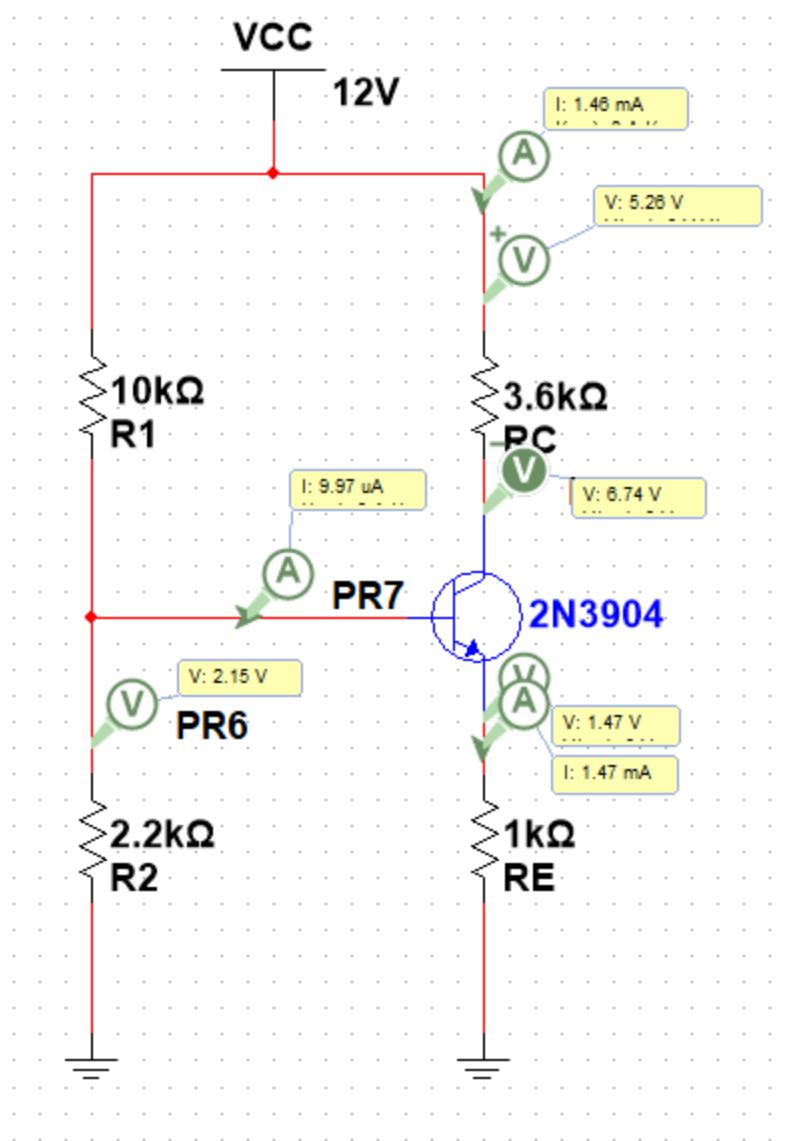


Figure 9

The following images are all the probe placements, as well as the measured value for  $V_B$ ,  $V_E$ ,  $V_C$ ,  $V_{RC}$ ,  $I_B$ ,  $I_C$ , and  $I_E$  at  $R_E = 2\text{k}\Omega$  respectively.

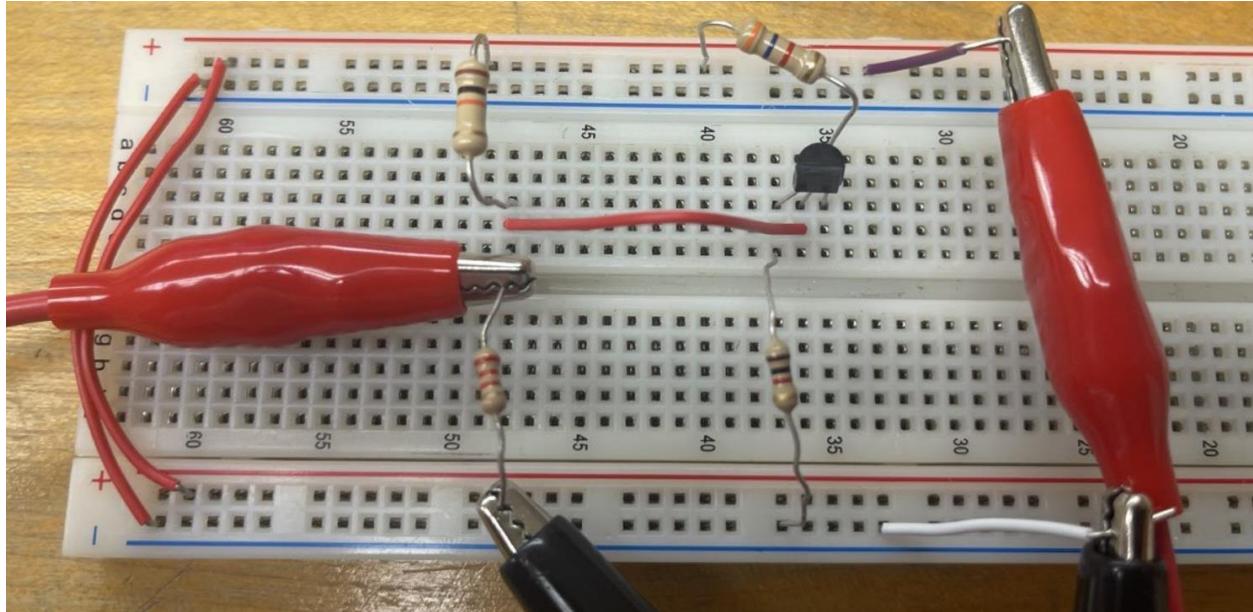
Figure 10 –  $V_B$ 

Figure 11

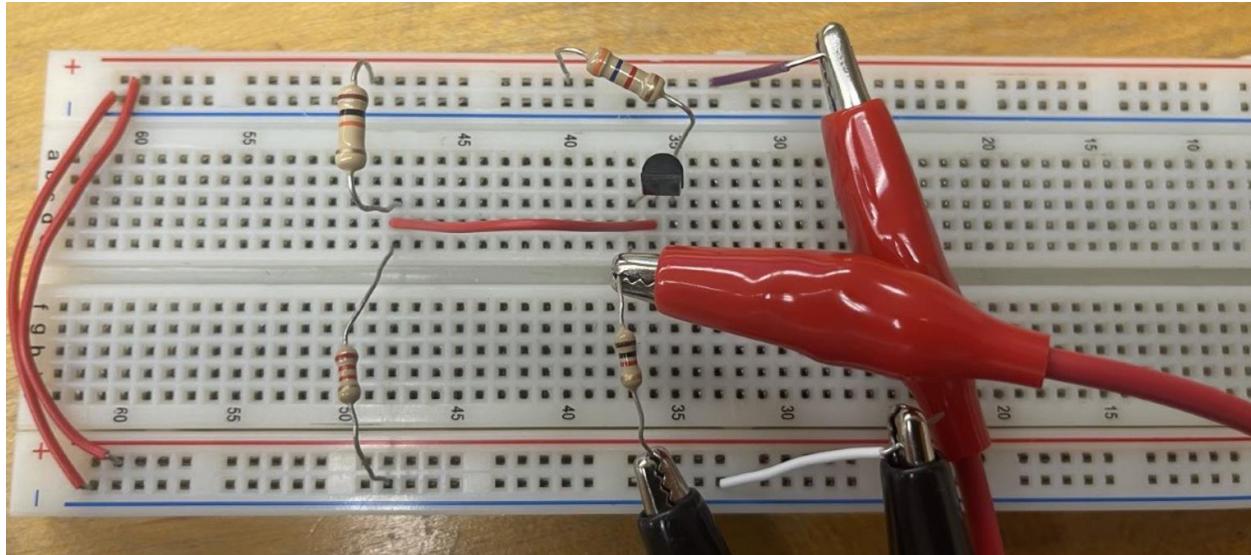


Figure 12

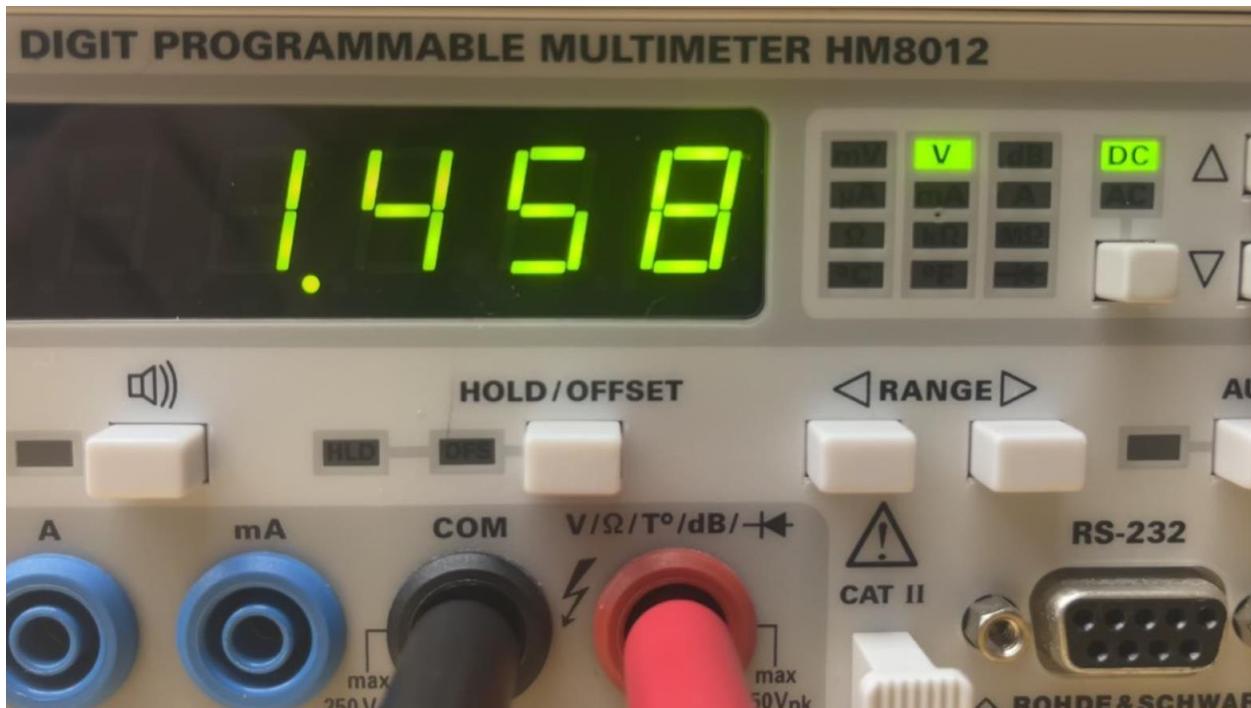


Figure 13

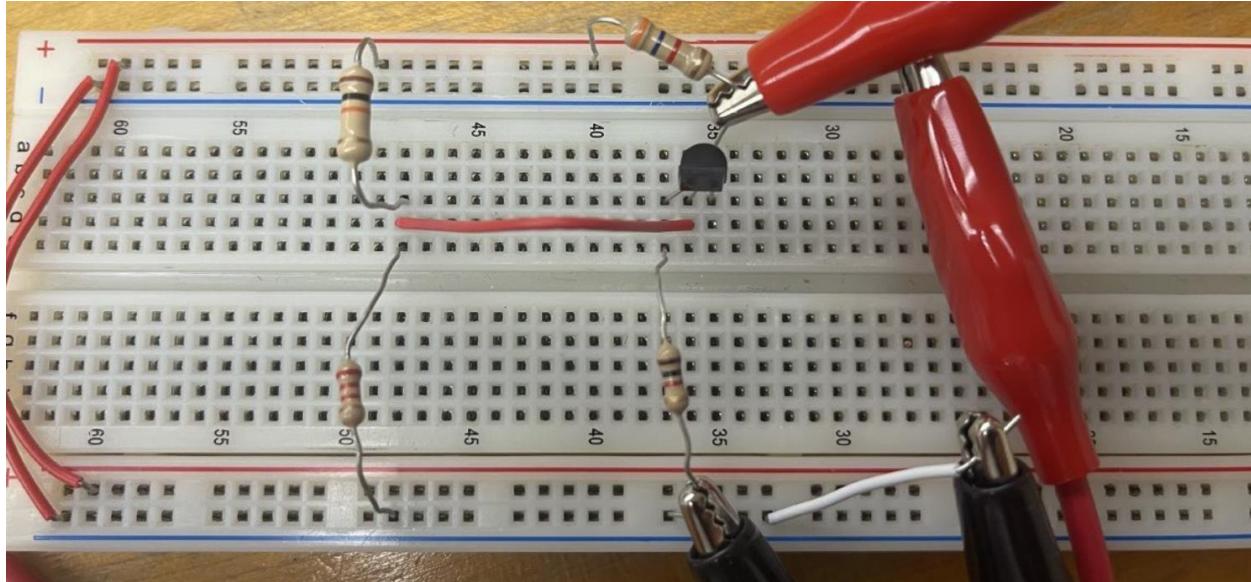


Figure 14



Figure 15

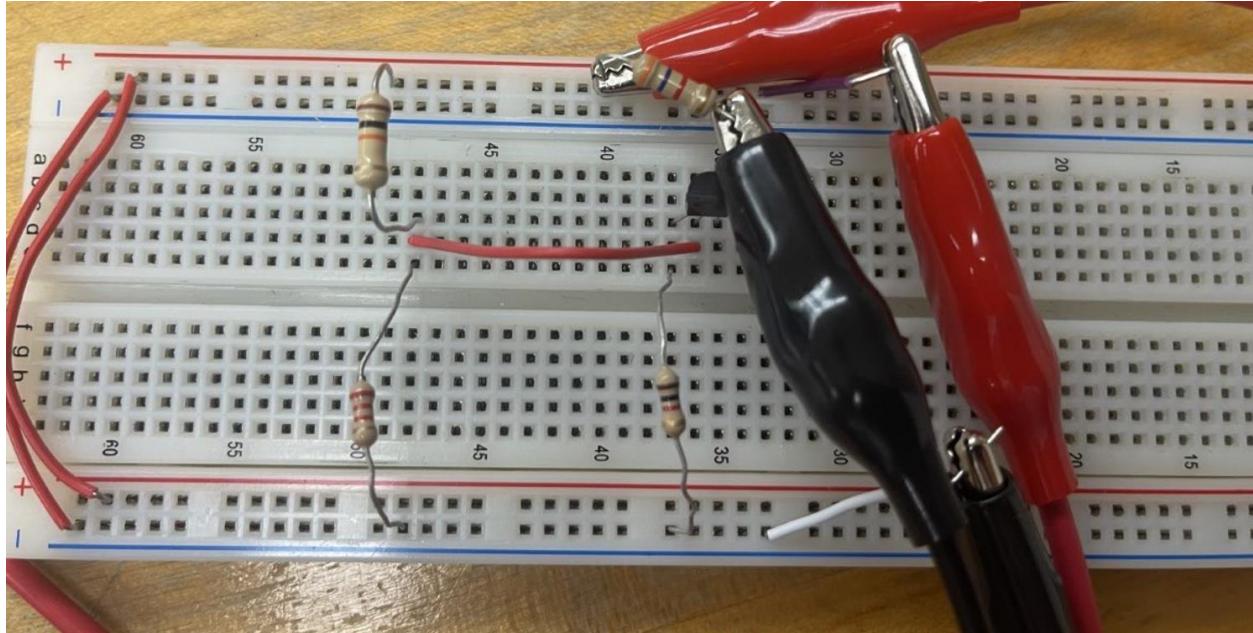


Figure 16



Figure 17

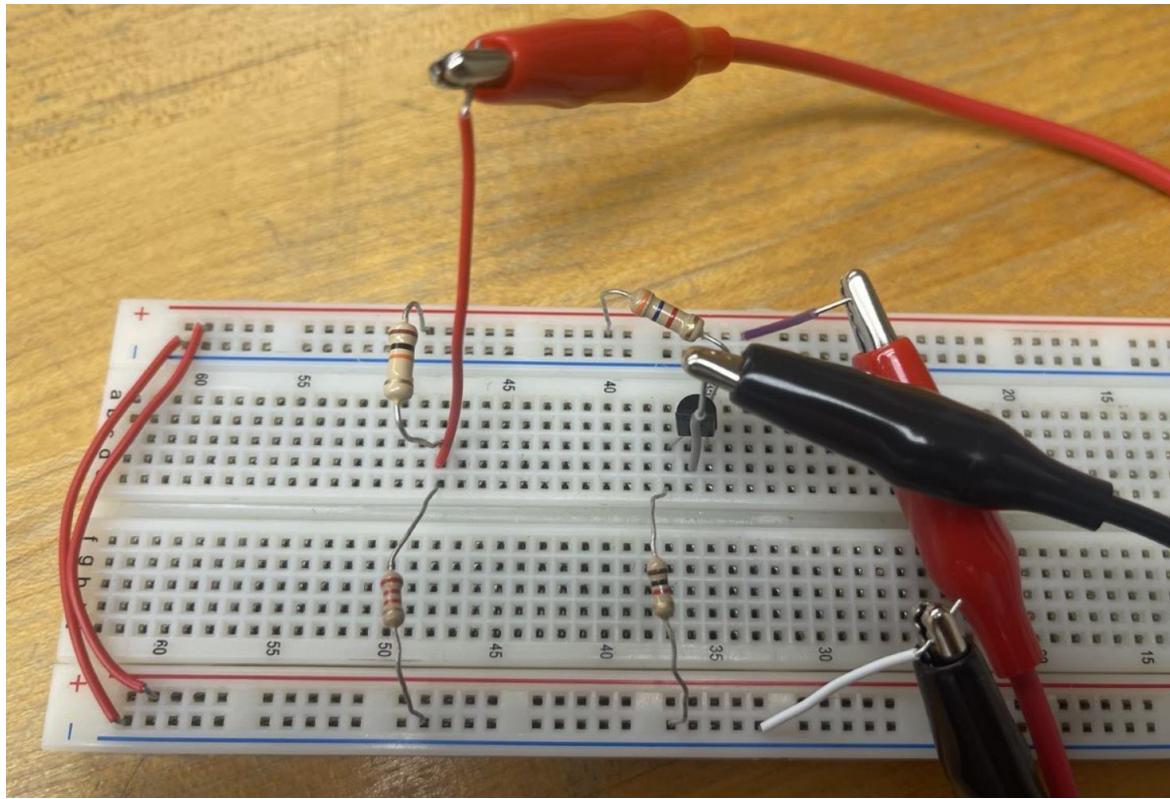


Figure 18



Figure 19

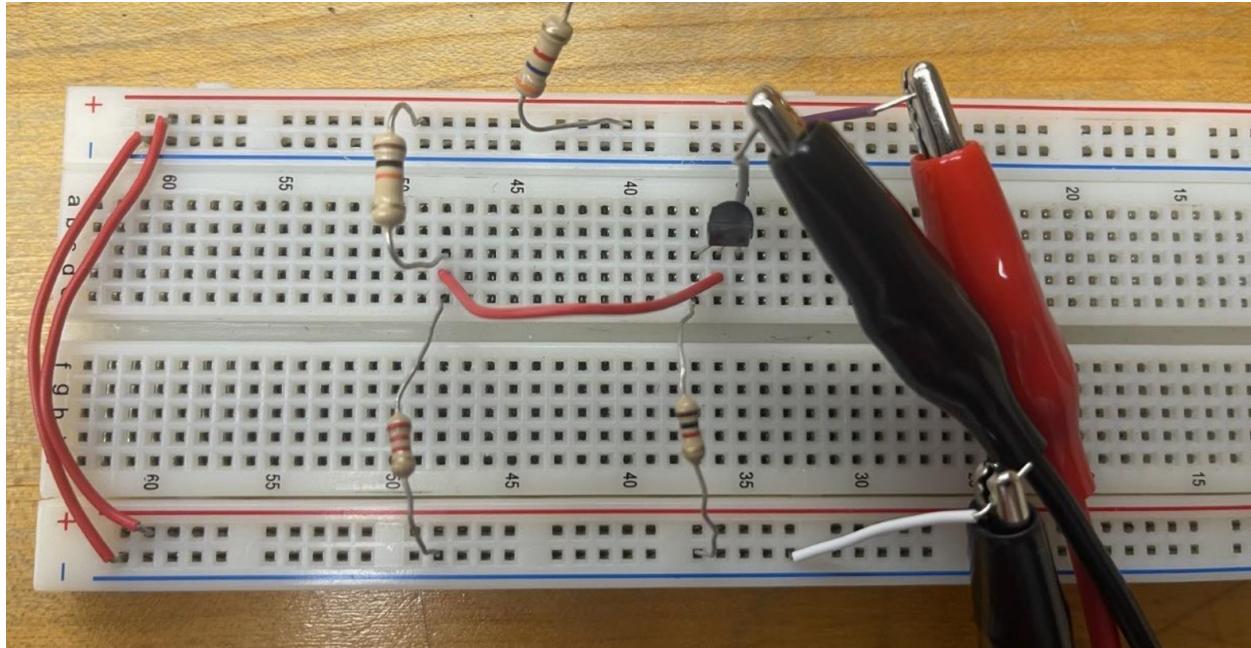


Figure 20



Figure 21

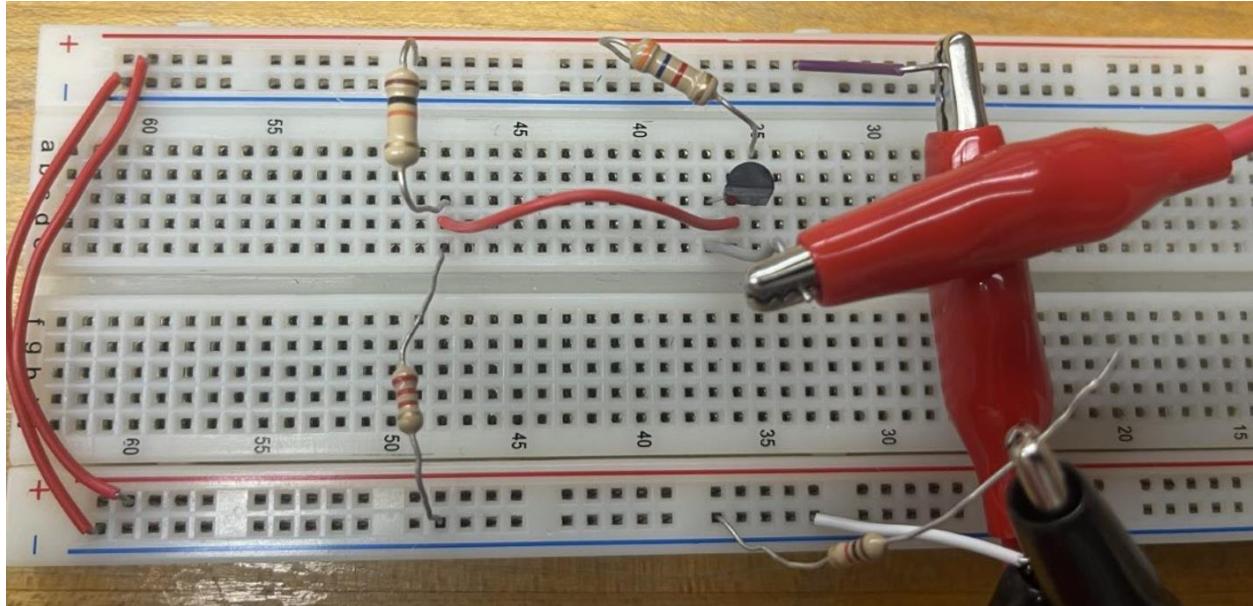


Figure 22



Figure 23

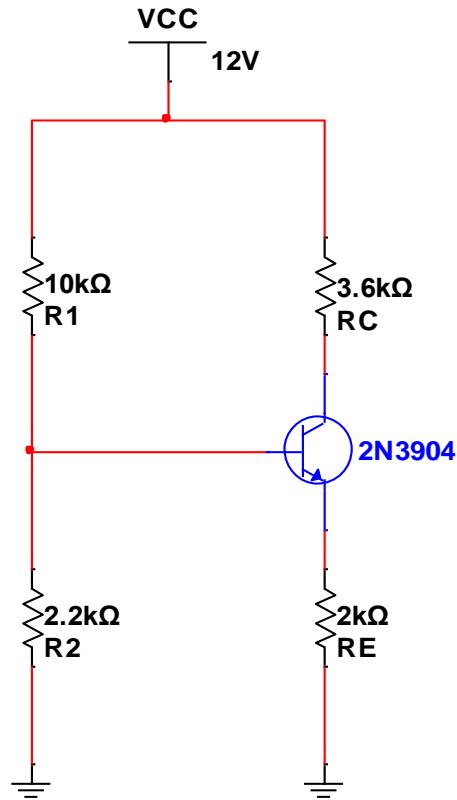


Figure 24

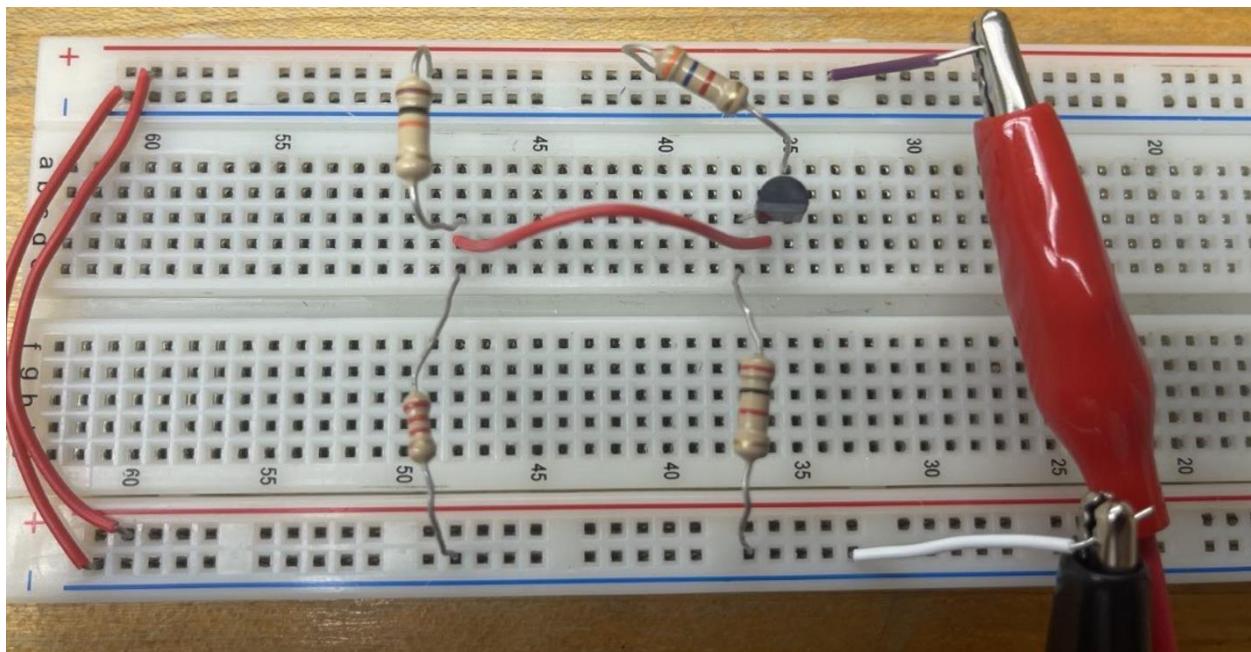


Figure 25

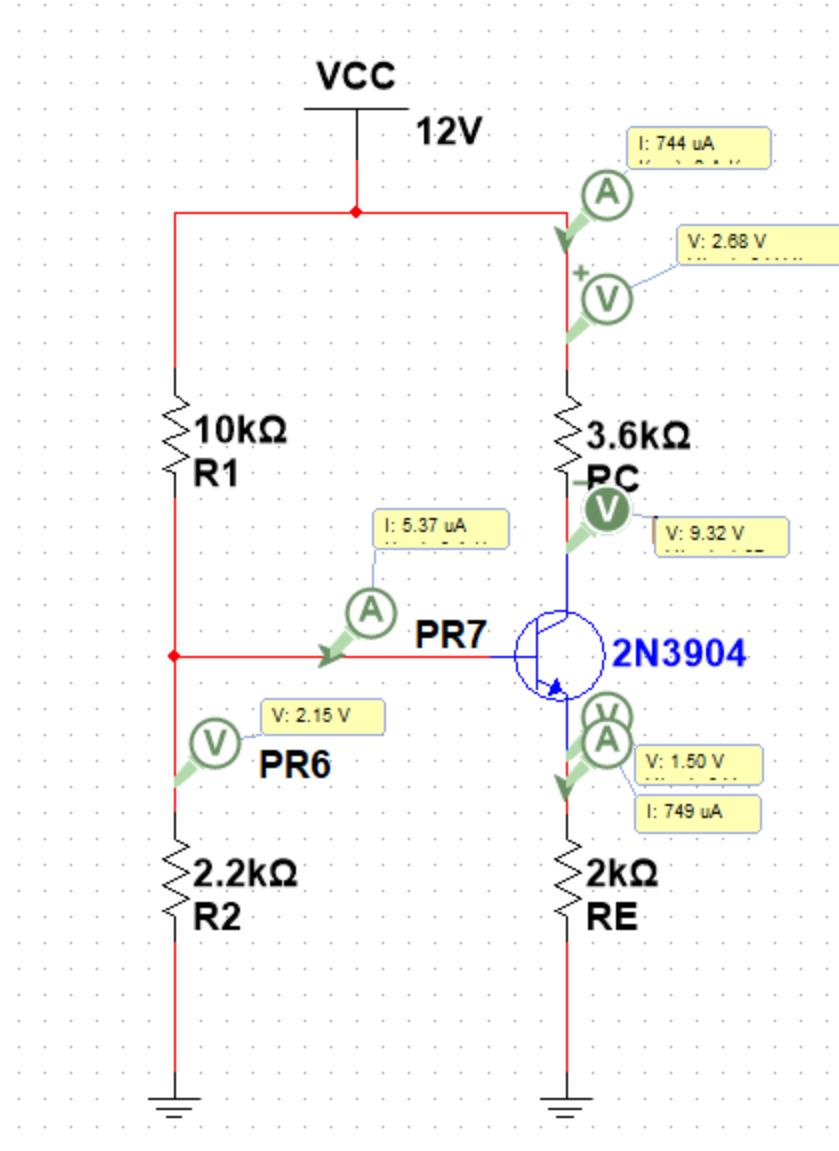


Figure 26

The following images are all the measuring probe placemets, as well as the measured value for  $V_B$ ,  $V_E$ ,  $V_C$ ,  $V_{RC}$ ,  $I_B$ ,  $I_C$ , and  $I_E$  at  $R_E = 2\text{k}\Omega$  respectively.

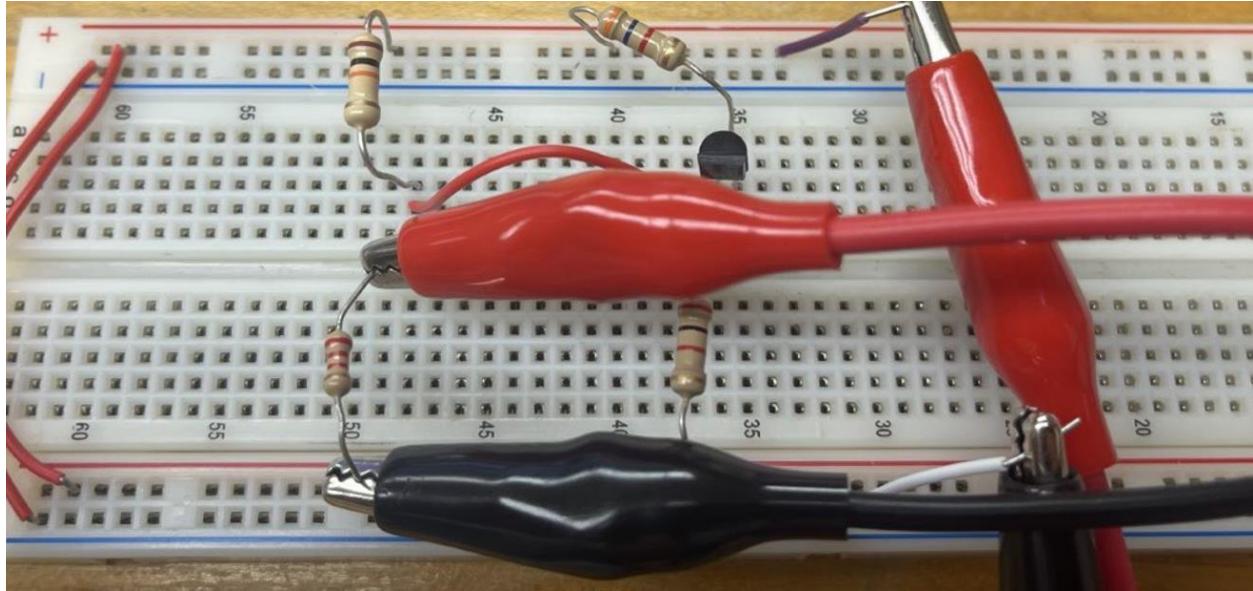


Figure 27



Figure 28

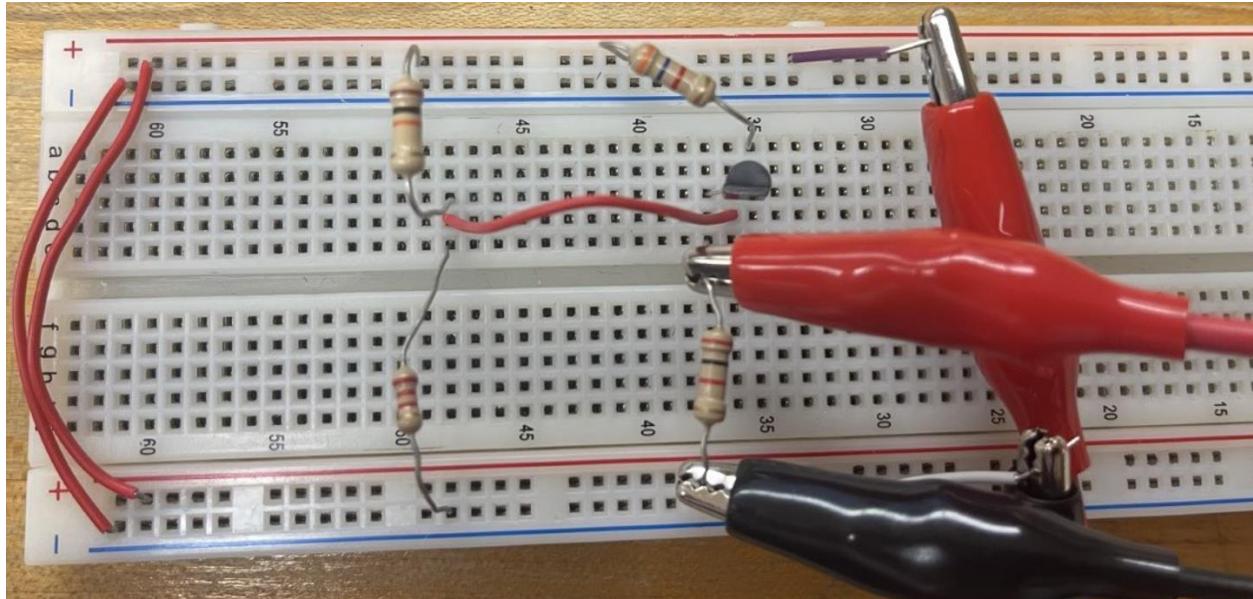


Figure 29


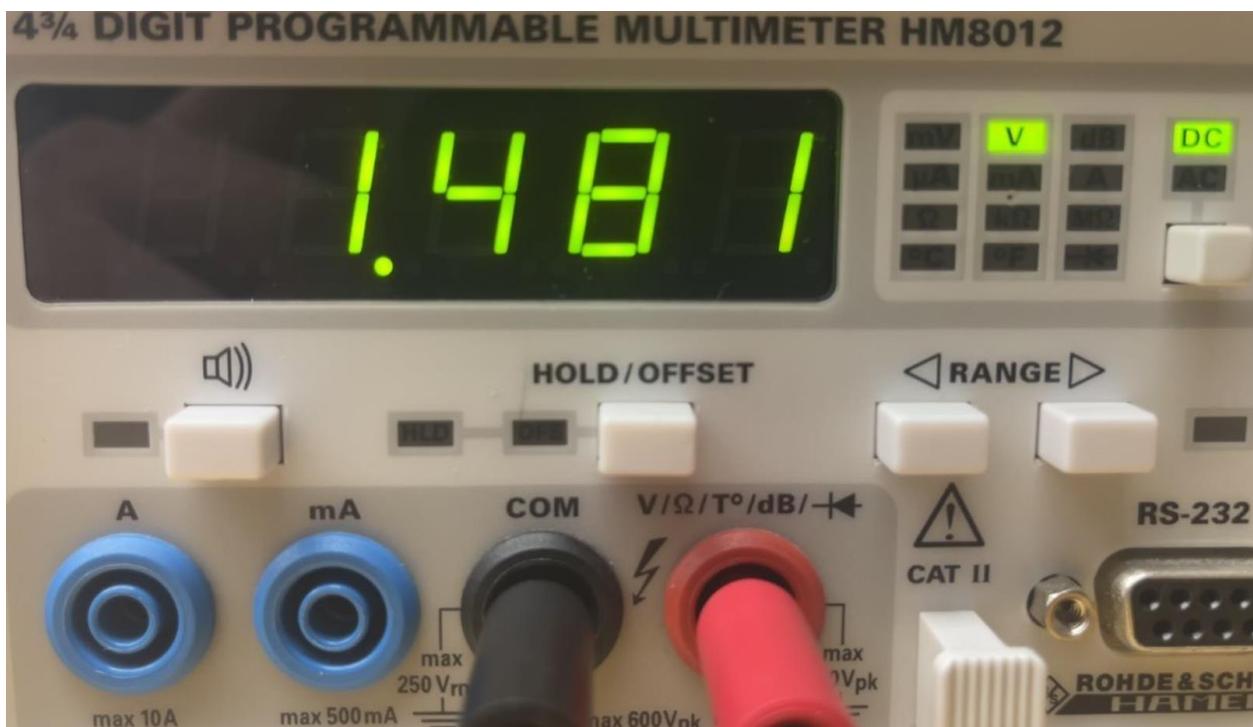


Figure 30

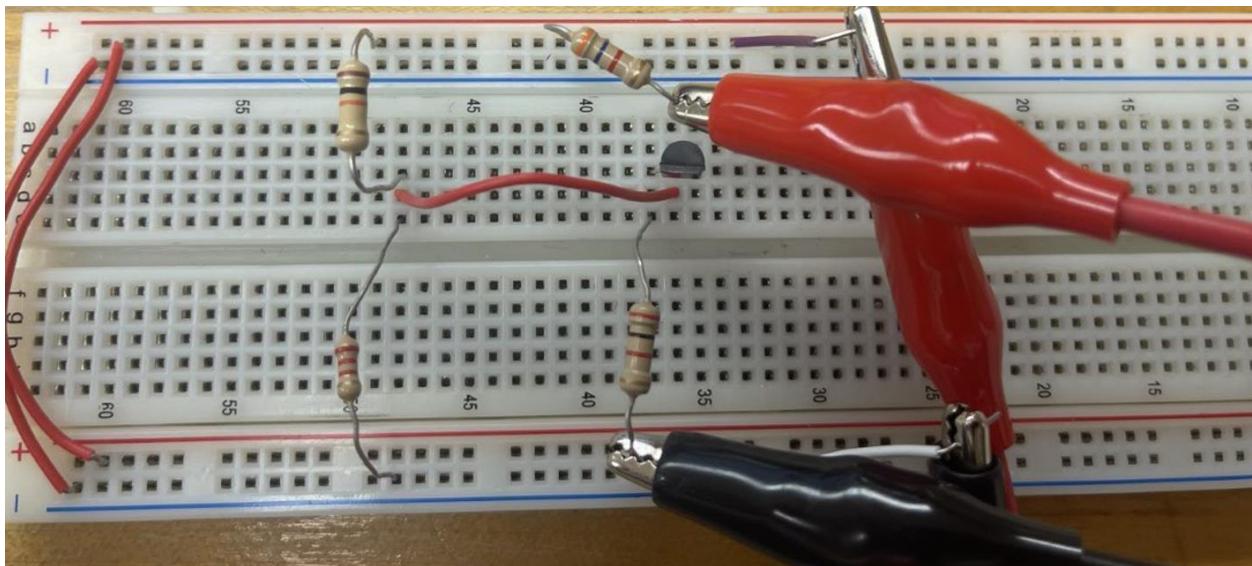

*Figure 31*



*Figure 32*

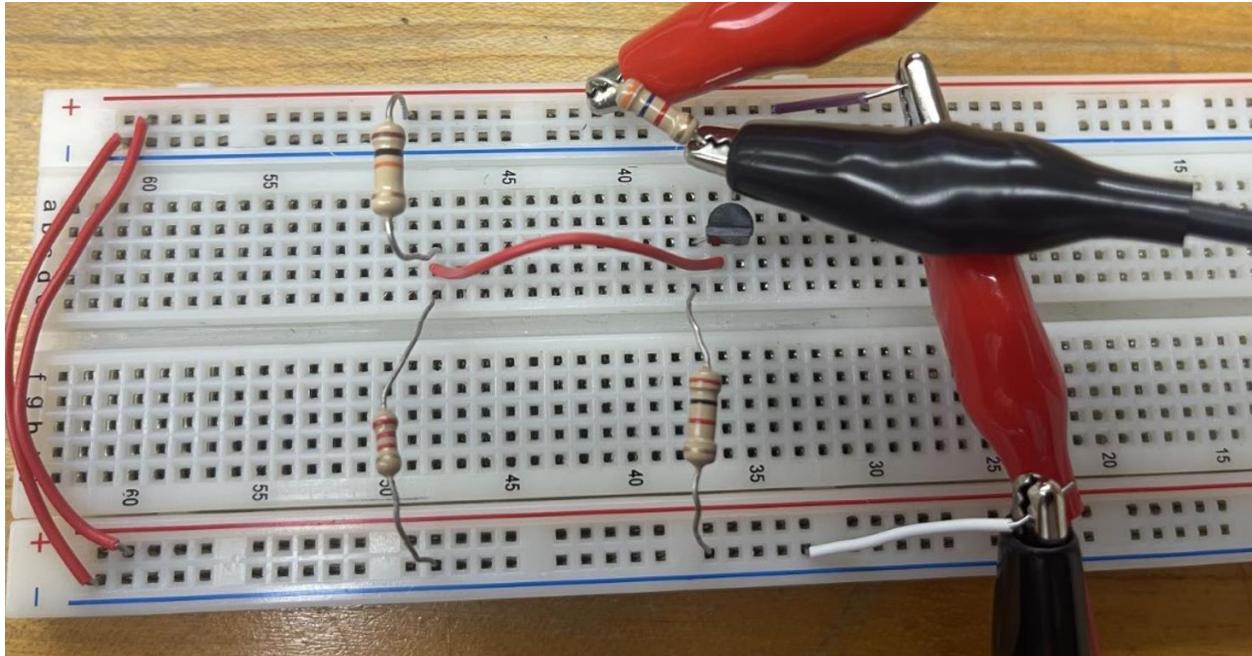


Figure 33



Figure 34

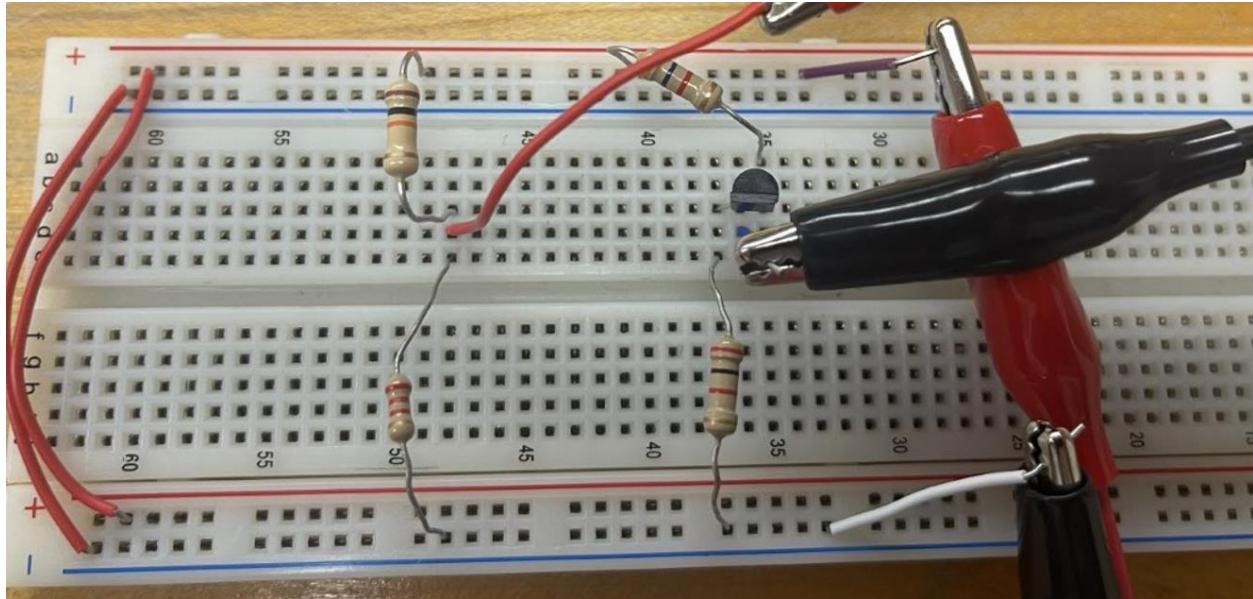


Figure 35



Figure 36

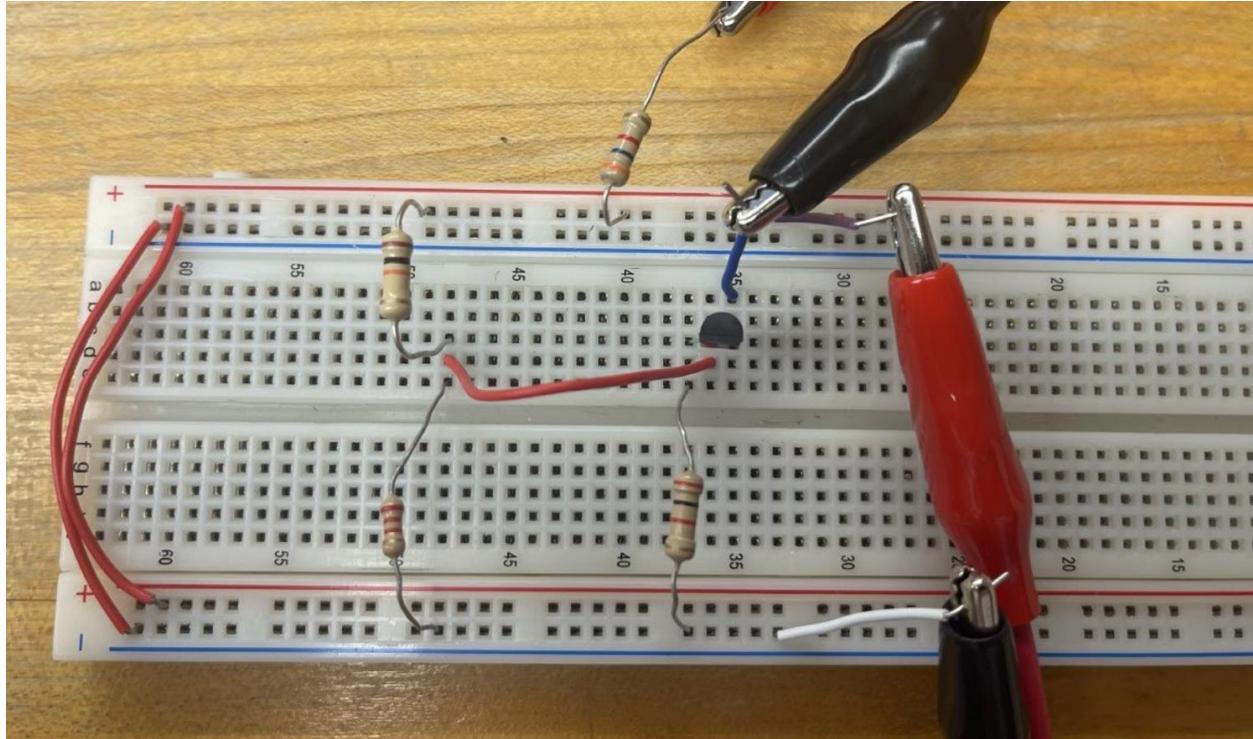


Figure 37



Figure 38

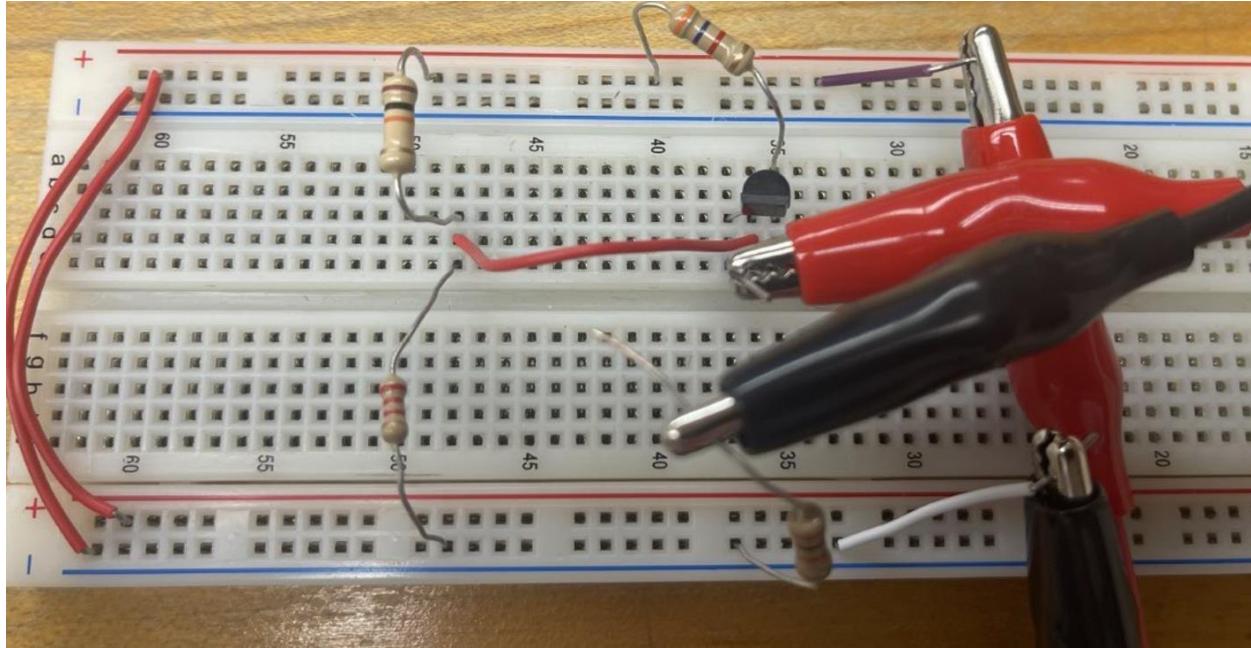


Figure 39



Figure 40

Furthermore, the beta ( $\beta$ ) of the transistor, which is a measure of its current gain, was assumed to be constant for theoretical calculations. However, in practice,  $\beta$  can vary significantly between individual transistors, even of the same model, and this variation can impact the circuit's behavior, which was an important observation during the lab exercises.

### Calculations for $R_E = 1 \text{ k}\Omega$

$$R_{INBASE} = \beta_{DC} * R_E = 150 * 1\text{k}\Omega = 150\text{k}\Omega$$

$$V_B = VCC * \frac{(R_2 \parallel R_{INBASE})}{R1 + (R_2 \parallel R_{INBASE})} = \frac{2.17\text{k}\Omega}{1\text{k}\Omega + 2.17\text{k}\Omega} = 2.13 \text{ V}$$

$$V_E = V_B - V_{BE} = 2.13\text{V} - 0.7\text{V} = 1.43 \text{ V}$$

$$I_E = \frac{V_E}{R_E} = \frac{1.43\text{V}}{1\text{k}\Omega} = 1.43 \text{ mA} \approx I_C$$

$$V_{RC} = I_C * R_C = 1.43\text{mA} * 3.6\text{k}\Omega = 5.148 \text{ V}$$

$$V_C = VCC - V_{RC} = 12\text{V} - 5.143\text{V} = 6.852 \text{ V}$$

$$I_B = \frac{I_C}{\beta_{DC}} = \frac{1.43\text{mA}}{150} = 9.53\mu\text{A}$$

$$\beta_{DC} = \frac{I_C}{I_B} = \frac{1.43 \text{ mA}}{9.53 \mu\text{A}} = 177.95$$

### Calculations for $R_E = 2\text{k}\Omega$

$$R_{INBASE} = \beta_{DC} * R_E = 150 * 2\text{k}\Omega = 300\text{k}\Omega$$

$$V_B = VCC * \frac{(R_2 \parallel R_{INBASE})}{R1 + (R_2 \parallel R_{INBASE})} = \frac{2.184\text{k}\Omega}{2\text{k}\Omega + 2.184\text{k}\Omega} = 2.151 \text{ V}$$

$$V_E = V_B - V_{BE} = 2.151\text{V} - 0.7\text{V} = 1.451 \text{ V}$$

$$I_E = \frac{V_E}{R_E} = \frac{1.451\text{V}}{2\text{k}\Omega} = 725 \mu\text{A} \approx I_C$$

$$V_{RC} = I_C * R_C = 725.5 \mu\text{A} * 3.6\text{k}\Omega = 2.612 \text{ V}$$

$$V_C = VCC - V_{RC} = 12\text{V} - 2.612\text{V} = 9.388 \text{ V}$$

$$I_B = \frac{I_C}{\beta_{DC}} = \frac{725.5 \mu A}{150} = 4.83 \mu A$$

$$\beta_{DC} = \frac{I_C}{I_B} = \frac{725.5 \mu A}{4.29 \mu A} = 171.67$$

**Table 2**

<b>Parameters</b>	<b>R<sub>E</sub> = 1kΩ Computed</b>	<b>R<sub>E</sub> = 1kΩ Measured</b>	<b>R<sub>E</sub> = 2kΩ Computed</b>	<b>R<sub>E</sub> = 2kΩ Measured</b>
V <sub>B</sub>	2.13V	2.144 V	2.151V	2.149 V
V <sub>E</sub>	1.43V	1.458 V	1.451 V	1.481 V
V <sub>C</sub>	6.852V	6.729 V	9.388 V	9.355 V
V <sub>RC</sub>	5.148V	5.27 V	2.612 V	2.628 V
I <sub>B</sub>	9.53μA	8.3 μA	4.83 μA	4.29 μA
I <sub>C</sub>	1.43mA	1.477 mA	725.5 μA	736.5 μA
I <sub>E</sub>	1.43mA	1.351 mA	725.5 μA	705.6 μA
β	150	177.95	150	171.67

When examining the effects of changing the emitter resistance (R<sub>E</sub>) from 1 kΩ to 2 kΩ, the data illustrated that a higher R<sub>E</sub> value resulted in a larger voltage drop across the emitter resistor, which in turn affected the V<sub>CE</sub> and I<sub>C</sub>.

The experiment provided practical confirmation of the theoretical characteristic curves for a BJT. Observing the shifts in operating points on the DC load line graphically demonstrated the influence of R<sub>E</sub> on the saturation and cutoff regions of transistor operation. This hands-on experience is invaluable for understanding how various components and their interconnections can affect the overall performance of electronic circuits.

The data also suggested that while the theoretical model is a crucial starting point, actual component tolerances and variations in transistor parameters can lead to deviations from calculated expectations. This reinforces the notion that while simulation tools like Multisim are beneficial for initial design and testing, there is no substitute for real-world experimentation where components exhibit natural variations.

## Experiment 7

### Bipolar Junction Transistors

#### Voltage Divider Biasing

Voltage Divider Biasing is another technique used to set up the DC operating point for an amplifier circuit. Voltage divider biasing is the most effective method in establishing a stable operating point (Q point) for the amplifier circuit. This biasing technique provides a constant base voltage in spite of any changes in the base current.

**Objective:** To investigate the operation of voltage divider biased circuit.

**Materials**

- One power supply
- 1k $\Omega$ , 2.2k $\Omega$ , 3.6k $\Omega$ , and 10k $\Omega$  Resistors
- BJT Transistor (2N3904)

Input: Power supply

Output: Multimeter

- 1- Build the voltage divider circuit shown in Figure 1.
- 2- Measure the value of each resistor and record in Table 1.
- 3- Compute and measure each parameter listed in Table 2.
- 4- Change the emitter resistance  $R_E$  value from 1 k $\Omega$  to 2 k $\Omega$  and repeat step 3.

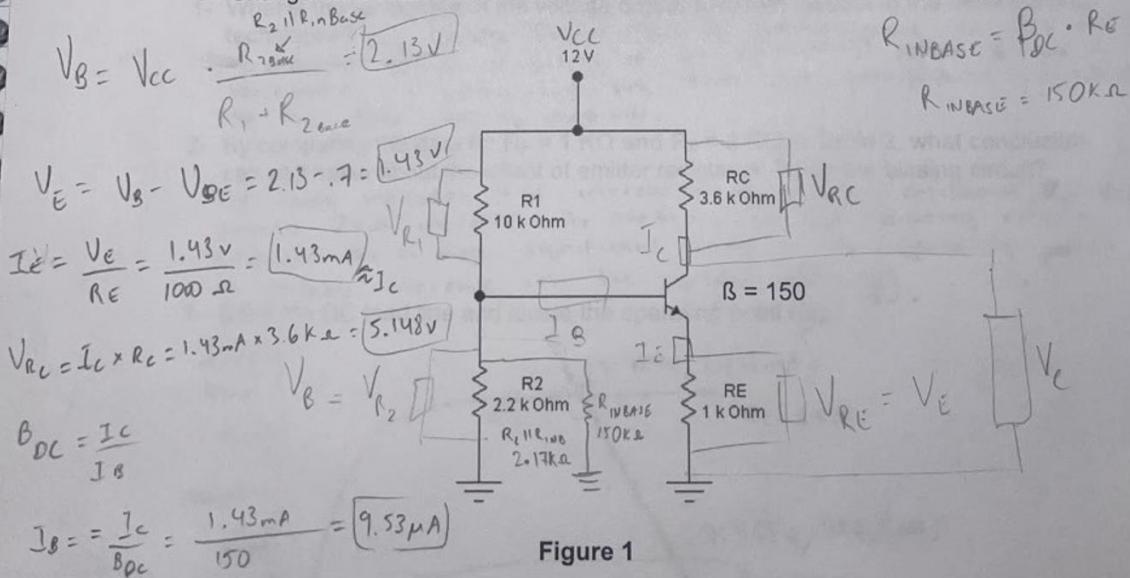


Figure 1

Resistor	Nominal	Measured
R <sub>1</sub>	10 kΩ	9.896 kΩ
R <sub>2</sub>	2.2 kΩ	2.172 kΩ
R <sub>c</sub>	3.6 kΩ	3.569 kΩ
R <sub>E</sub>	1 kΩ	981.5 Ω

B 3.13.24


Table 1

$$\beta_{DC} = \frac{I_C}{I_B}$$

Parameter	R <sub>E</sub> = 1 kΩ		R <sub>E</sub> = 2 kΩ	
	Computed	Measured	Computed	Measured
V <sub>B</sub>	2.13 V	2.144 V	2.151 V	2.149 V
V <sub>E</sub>	1.43 V	1.458 V	1.451 V	1.481 V
V <sub>C</sub>	6.852 V	6.729 V	9.388 V	9.355 V
V <sub>RC</sub>	5.148 V	5.27 V	2.612 V	2.628 V
I <sub>B</sub>	9.53 mA	8.3 mA	4.83 mA	4.29 mA
I <sub>C</sub>	1.43 mA	1.477 mA	725.5 mA	736.5 mA
I <sub>E</sub>	1.43 mA	1.351 mA	725.5 mA	705.6 mA
β		177.95		171.67

Table 2

- What is the advantage of the voltage divider bias with respect to the other biasing techniques? The Voltage Divider bias is advantageous for its ability to provide better stability of the transistor's operating point against variations in temperature and transistor beta(β) value compared to the other biasing methods.
- By comparing the data for R<sub>E</sub> = 1 kΩ and R<sub>E</sub> = 2 kΩ in Table 2, what conclusion can you make about the effect of emitter resistance R<sub>E</sub> on the biasing circuit? The data indicates that increasing the Emitter resistance R<sub>E</sub> from 1kΩ to 2kΩ increases the stability of the biasing circuit, evidenced by a more significant shift in the operating point and a notable increase in the current gain (β).
- Draw the DC load line and locate the operating point (Q).

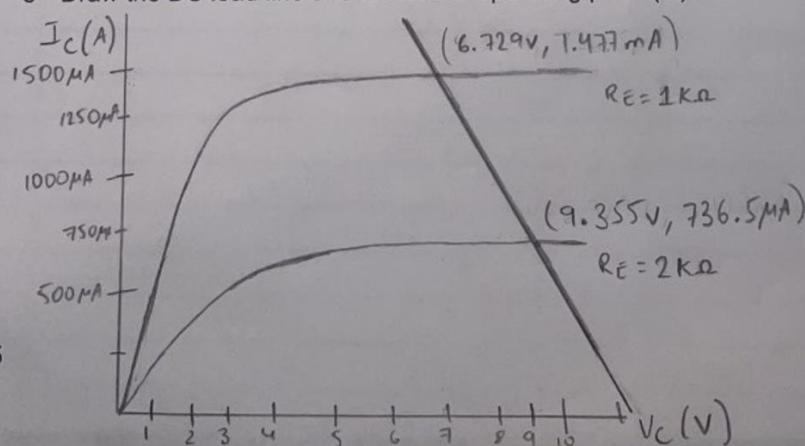

**Conclusion:**

The lab aimed to investigate the operation of a voltage divider biased circuit and its effects on the stability of a bipolar junction transistor's (BJT) operating point. This objective was successfully met, as we constructed the circuit, measured its parameters, and compared the results against theoretical predictions. The lab facilitated a deeper understanding of how changes in the emitter resistance ( $R_E$ ) affect the transistor's behavior, reinforcing the theory that a higher  $R_E$  can enhance the stability of the operating point. Additionally, we observed the real-world implications of component tolerances and their effects on circuit performance. The insights gained from the discrepancies between calculated and actual measurements underpin the importance of considering practical variances in the design and analysis of electronic circuits. Overall, the lab was effective in bridging theoretical knowledge with practical application, providing a solid foundation for future electronic design endeavors.